

GUJARAT TECHNOLOGICAL UNIVERSITY**M.E –IIst SEMESTER–EXAMINATION – JULY- 2012****Subject code: 1720705****Date: 10/07/2012****Subject Name: Application of Power Electronics in Power Systems****Time: 10:30 am – 13:00 pm****Total Marks: 70****Instructions:**

- 1. Attempt all questions.**
- 2. Make suitable assumptions wherever necessary.**
- 3. Figures to the right indicate full marks.**

- Q.1** (a) Derive an expression for mid-point voltage of a symmetrical lossless transmission line as a function of power flow on it. **07**
- (b) Explain the FC-TCR configuration. Explain operating characteristic without step down transformer and losses in FC-TCR. **07**

- Q.2** (a) Explain Thyristor Controlled Transformer. **07**
- (b) Explain the basic working principle of UPFC. **07**

OR

- (b) Explain (a) Load Compensation and (b) System Compensation and its effect on transmission line and load side. **07**

- Q.3** (a) For a given 1000 kV, 50 Hz, 1000 km long, symmetrical transmission line with $l = 0.85$ mH/km, $c = 13.5$ nF/km mid- point compensated line, the operating load angle δ can be varied from 20° to 58° . Find the MVAR capacity range for unlimited var compensator. V_{mc} is to be held at 1.02 pu. Also comment on result. **07**
- (b) Explain with the help of suitable diagram working principle of STATCOM and its VI characteristic. **07**

OR

- Q.3** (a) For a given 765 kV, 50 Hz, 750 km long, symmetrical transmission line with $l = 0.9$ mH/km, $c = 12.1$ nF/km mid- point compensated line, find uncompensated real power (P_s), compensated real power (P_{comp}) with unlimited capacity compensator at midpoint with maintained mid point voltage to be 1.03 pu and injected reactive power (Q_v). The value of load angle δ is 35° . Also comment on results. **07**
- (b) Define SSR. What is the significance of SSR mitigation. **07**

- Q.4** (a) Explain effect of power-transfer capacity for series compensator. **07**
- (b) Define and explain following in brief. **07**
- a). TCR b). TSC, c). TSSR, d). FACTS

OR

- Q.4** (a) Show that for the operating load angle $\delta=35^\circ$, the var net rating of the series compensator is around 10% of that required of a shunt compensator for the same change in power transfer. **07**
- (b) Explain different practical switching strategies with the help of capacitor current, capacitor voltage and supply voltage waveforms for TSC. **07**

- Q.5** (a) Explain Harmonic performance of TCSC. **07**
- (b) Draw and explain the block diagram of a typical TCSC power control structure. **07**

- Q.5** (a) Derive expression of net reactance of the TCSC in per units of the nominal reactance of the fixed capacitor (X_C). **07**
- (b) Discuss TCSC impedance at sub-synchronous frequencies. **07**
