

GUJARAT TECHNOLOGICAL UNIVERSITY**M.E –IIst SEMESTER–EXAMINATION – JULY- 2012****Subject code: 1720707****Date: 12/07/2012****Subject Name: Flexible AC Transmission System****Time: 10:30 am – 13:00 pm****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

- Q.1** (a) List the FACTS devices. Give a classification of series and shunt FACTS devices. Mention the advantages of FACTS devices. **07**
- (b) Prove that the midpoint shunt compensation can almost double the power transfer capability of a transmission line. **07**

- Q.2** (a) Explain the construction and working of a Static Voltage Compensator (SVC) **07**
- (b) Briefly describe Sub-Synchronous Resonance. Discuss the application of a TCSC for SSR mitigation. **07**

OR

- (b) Mention the modes of operation of a TCSC. Describe the Vernier Capacitive mode of operation in detail with steady state waveforms of voltages and currents. **07**

- Q.3** (a) Discuss the application of SSSC as a reactive power controller. Draw and discuss the necessary control circuit. **07**
- (b) With neat power circuit diagram, describe the 6-pulse voltage source converter type STATCOM **07**

OR

- Q.3** (a) Draw the necessary block diagram and describe the application of an SSSC for power swing damping. **07**
- (b) Justify the statement “STATCOM can be used as a midpoint shunt compensator for a transmission line” **07**

- Q.4** (a) Explain the construction and working of a Unified Power Flow Controller (UPFC). **07**
- (b) With suitable diagram describe the Thyristor Controlled Reactor (TCR) also discuss its applications in the power system. **07**

OR

- Q.4** (a) Mention the methods of passive reactive power compensation. Compare them with compensation using FACTS devices. **07**
- Q.4** (b) Mention the advantages of having slope in the dynamic characteristics of a SVC. **07**

- Q.5** (a) Discuss the role of SVC as a voltage controller. **07**
- (b) Draw and discuss the firing delay angle versus the net fundamental reactance characteristic of a TCSC. **07**

OR

- Q.5** (a) Explain the operating characteristic of FC-TCR. **07**
- (b) Briefly describe the working of a Thyristor Controlled Transformer (TCT). **07**
