Seat No.: Enrolment No GUJARAT TECHNOLOGICAL UNIVERSITY		D.: Enrolment No	
		GUJARAT TECHNOLOGICAL UNIVERSITY	
		M.E –IIst SEMESTER–EXAMINATION – JULY- 2012	
,	Subje	ct code: 1724502 Date: 09/07/201	12
;	Subje	ct Name: Power Electronics-II	
	•	10:30 am – 13:00 pm Total Marks: 7	70
		uctions:	
		Attempt all questions.	
		Make suitable assumptions wherever necessary.	
	3.	Figures to the right indicate full marks.	
0.1	()	The decomplication of multi-multi-mass and multi-mass in data.	0.5
Q.1		List the application of multilevel inverter and explain one in detail.	07
	(b)	Explain half bridge series resonant inverter with unidirectional switches.	07
Q.2	(a)	Derive formula of power factor for non linear load and explain in terms.	07
~ ·-	(b)	Explain the frequency response of parallel loaded resonant inverter.	07
	` ,	OR	
	(b)	Explain the full bridge series resonant inverter with bidirectional switches in non	07
		overlapping mode.	
0.3	(a)	Explain H-bridge 5-level Inverter.	07
Q.3		Explain zero voltage switching (ZVS) resonant converter.	07
	(b)	OR	U/
Q.3	(a)	Derive the formula for instantaneous current in series resonant inverter. Also	07
	` '	derive the time required to reach peak value of current.	
	(b)	The full bridge series resonant inverter with unidirectional switches has $L = 45 \mu H$,	07
		$C = 7 \mu F$, and $R = 4 \Omega$. The frequency of output voltage is 4.5 kHz and DC input is	
		200 Volt. SCR turn off time is 15 μSec. Calculate:	
		(a) Circuit turn off time,	
		(b) Maximum possible output frequency and	
		(c) Capacitor voltage.	
Q.4	(a)	Explain buck boost topology for PFC converter.	07
	(b)	Explain with diagram different types of active power filter.	07
		OR	
Q.4	(a)	Draw and explain how single phase PFC topology can be used to implement three	07
	(1.)	phase PFC solution.	0=
	(b)	•	07
		12 pulse series type diode rectifier.	
Q.5	(a)	Explain the steps to design the inductor used in dc-dc converter.	07
	(b)	Discuss the selection factor for the magnetic component.	07
	` ,	OR	
Q.5	(a)	Discuss the steps to design EMI filter.	07
	(b)	What is a matrix converter? Explain with three phase circuit supplying three phase	07
		load.	
