Enrolment No._

GUJARAT TECHNOLOGICAL UNIVERSITY

M.E –Ist SEMESTER–EXAMINATION – JULY- 2012

Subject code: 710702N

Subject Name: Advanced Power Electronics

Date: 07/07/2012

Total Marks: 70

Time: 2:30 pm – 05:00 pm

Instructions:

- 1. Attempt all questions.
- 2. Make suitable assumptions wherever necessary.
- 3. Figures to the right indicate full marks.
- Q.1 (a) Discuss different constructional features of GTO'S with switching 07 characteristics curves, and explain relative comparison of GTO'S and SCR.
 - (b) Describe the necessity of Isolation of gate and Base drives and explain how 07 they are implemented using the pulse transformer and Opto Isolator with necessary circuit diagrams.
- Q.2 (a) What is PWM Inverter principle? List the different pulse width modulation 07 techniques used for inverters? Describe Multiple Pulse Modulation technique of PWM inverter with necessary waveforms and harmonic spectrums.
 - (b) Describe the phase angle control techniques for AC Voltage controllers and 07 Derive the expression for rms and average value of output voltage for $1-\emptyset$ half wave AC voltage controller.

OR

- (b) With neat circuit and waveforms explain three phase current source 07 transistorized Inverter and compare with voltage source inverter.
- Q.3 (a) Explain the principle of operation of three phase bridge inverter with 150° 07 conduction mode with necessary circuit diagram and waveforms.
 - (b) What is switching mode regulator? List the basic types of switching mode 07 regulators. Explain in brief Forward converter with necessary circuit diagram and waveforms.

OR

- Q.3 (a) Draw the neat circuit diagram of three phase full wave bidirectional AC 07 Voltage controller and explain it's working with waveforms for different firing angles.
 - (b) The three phase full wave controller supplies a star connected resistive load 07 of $R = 10 \Omega$ and the line –to line input voltage is 208 volt (rms), 60 Hz. The delay angle is $\alpha = \pi/3$. Determine (a) The RMS output voltage Vo (b) The input power factor and (c) the expression for the instantaneous output voltage of phase a.
- Q.4 (a) Give different circuit configurations for base drive of BJT. 07
 - (b) Explain the various protection circuits against dv/dt, di/dt and overvoltage in 07 the driver circuit of power devices.

- Q.4 (a) Discuss various harmonics reduction techniques in the Inverter output with 07 necessary sketches
 - (b) Describe Buck converter and obtain necessary derivations for continuous 07 mode of conductions.
- Q.5 (a) Explain with neat circuit diagram and waveforms the principle of operation 07 of three phase half wave cyclo converters with circulating current mode and discuss the advantages of circulating current mode..
 - (b) Discuss salient features of IGBT with it's transfer characteristics 07

OR

- Q.5 (a) Explain operation of Multi output switch mode regulator with circuit 07 diagram and timing diagram.
 - (b) Describe the high frequency transformer design for fly back converter with 07 it's topology and waveforms.
