Seat No.: Enrolment No				
Scarr		GUJARAT TECHNOLOGICAL UNIVERSITY	_	
		M.E –I <sup>st</sup> SEMESTER–EXAMINATION – JULY- 2012		
Subject code: 713101N			Date: 05/07/2012	
•		lame: Medical System Design		
Time: 2:30 pm – 05:00 pm Total Marks				
Instr				
1.	Atte	empt all questions.		
		ke suitable assumptions wherever necessary.		
3.	Figi	ares to the right indicate full marks.		
Q.1	(a)	Give the assumptions taken during the analysis of LVDT. Explain the principle and working of the same with neat sketches.	07	
	<b>(b)</b>	Explain ultrasonic flow meter with neat sketches.	07	
Q.2	(a)	Explain the signal conditioning of thermocouple temperature measurement.	07	
	<b>(b)</b>	Explain the signal conditioning requirement of electromagnetic flow meter. <b>OR</b>	07	
	<b>(b)</b>	Enumerate the criteria for designing the multi channel high level data acquisition system.	07	
Q.3	(a)	Analyze the five Op-Amp instrumentation amplifier for biomedical signals with necessary derivations for design and diagrams	07	
	<b>(b)</b>	Explain the working of sample and hold devices in detail.  OR	07	
Q.3	(a)	Give the design consideration and selection criteria for acceleration measurement.	07	
	<b>(b)</b>	Design a power supply with following specifications:	07	
		Input voltage- 230V ± 10%, Input current 5Amp.maximum,		
		Output Voltage- 15 V, Output Current- 3 A		
Q.4	(a)	Explain the measurement of torque with neat sketches.	07	
	<b>(b)</b>	Give the transformer design for forward converter.  OR	07	
	(a)	What are the factors creating the hurdles in design of precise AC current source. Give practical remedies for the same.	07	
Q.4	<b>(b)</b>	Explain the scheme for surge current protection in biomedical circuits.	07	

(a) Explain the scheme for measurement of velocity with neat sketches.

(a) Explain forward converter in detail.

Give design consideration and selection criteria for stress measurement.

OR

Q.5

Q.5

1

**07** 

**07** 

**07** 

**07**