Se	eat N	o.: Enrolment No	
		GUJARAT TECHNOLOGICAL UNIVERSITY M.E -I <sup>st</sup> SEMESTER-EXAMINATION - JULY- 2012	
			2
	•	ect Name: Power Electronics-I	_
·			70
		uctions:	DGICAL UNIVERSITY MINATION – JULY- 2012 Date: 05/07/2012  Total Marks: 70  eccessary.  For MOSFET.  The neat circuit diagram and draw all the 107  rive its Average & RMS Output Voltage 107  For and Derive its Average 107  For and Derive its Averag
L		Attempt all questions.	
		Make suitable assumptions wherever necessary.	
		Figures to the right indicate full marks.	
Q.1		Explain the vertical cross section of power MOSFET.	07
	<b>(b)</b>	Explain the push-pull converter with neat circuit diagram and draw all the waveform related to the circuit.	07
Q.2	(a)	Explain Buck-Boost Converter and derive its Average & RMS Output Voltage Equation.	07
	<b>(b)</b>	Explain Full Bridge Forward converter and Derive its Average Output Voltage Equation.	07
		OR	
	<b>(b)</b>	For the 1-phase Half bridge Forward inverter has a resistive load of R=100 $\Omega$ and dc input voltage is 100 volt. Determine: (i) the RMS output voltage at the fundamental frequency, (ii) the output power Po, (iii) the average, RMS and Peak current through each transistor, (iv) THD.	07
Q.3	(a)	Explain 3-phase bridge inverter in 180 degree conduction mode and draw it's output phase and line voltage wave form with resistive load.	07
	<b>(b)</b>	Explain Sinusoidal PWM technique in detail.	07
		OR	
$\Omega$	(a)	Explain advantage and disadvantage of PWM technique	07

**Q.3** Explain advantage and disadvantage of PWM technique.

What is an ideal power semiconductor switch? State the requirements of gate 07 driver circuit for MOSFET.

**Q.4** (a) Explain the parallel operation of SCR. Discuss the equalizing methods for smooth 07 parallel operation.

**07** 

(b) Describe the operation of single phase full-wave A.C. Voltage regulator with R load with the help of voltage and current waveforms. Also, derive expression for RMS value of output voltage.

OR

Design dynamic equalizing network for proper operation of series connected SCR. 0.4 **07 07** 

With neat and clean waveform explain the principle of phase control. **(b)** 

**Q.5** (a) Explain the needs of Heatsink. Explain its selection process.

Explain the steps to design an inductor for converter application. **(b)** 

**07 07** 

OR

(a) Explain the six pulse diode converter supplying resistive load. **Q.5** 

**07** 

(b) Explain the changes required in power diode design to increase its voltage 07 withstand capacity as compared to signal diode.

\*\*\*\*\*