Seat N	lo.:	Enrolment No	_
<b>GUJARAT TECHNOLOGICAL UNIVERSITY</b>			
M.E –I <sup>st</sup> SEMESTER–EXAMINATION – JULY- 2012 Subject code: 714502N Date: 07/0			12
Time	Subject Name: Solid State DC Drives Time: 2:30 pm – 05:00 pm Instructions:  Total Marl		70
1. Attempt all questions.			
<ol> <li>Make suitable assumptions wherever necessary.</li> <li>Figures to the right indicate full marks.</li> </ol>			
Q.1	(a)	What is the effect of back-emf on the firing angle and avg. output voltage? Draw necessary waveforms.	07
	(b)	What is the difference between dynamic braking and regenerative braking? Write down the expressions for the average output voltage for step down and step up chopper.	07
Q.2	(a)	Explain operation of DC motor in forward motoring and forward braking with proper type of chopper. Explain both quadrant operations with appropriate wave forms.	07
	<b>(b)</b>	Draw equivalent circuit and output voltage waveform of an ideal dual converter. derive necessary condition of firing angles.  OR	07
	<b>(b)</b>	Develop transfer function of speed control of DC motor with PI controller and current control loop.	07
Q.3	(a)	Write a program flow chart for speed control of DC motor with current control.	07
	<b>(b)</b>	Why PLL is better for speed control of DC motor. Explain basic PLL operation.	07
Q.3	(a)	Develop a transfer function of separately excited DC motor with speed control loop. Give the limitation of only speed control loop.	07
	<b>(b)</b>	Develop a linearized transfer model of DC series motor.	07
Q.4	(a)	Explain the principle of phase control. Obtain the equation of output voltage of phase controlled dc motor drive.	07
	<b>(b)</b>	Explain the speed control of dc series motor using tap changing transformer and uncontrolled rectifier.  OR	07
Q.4	(a)	A 220 volt, 960 rpm, 12.8 A separately excited dc motor has armature resistance and inductance of 2 ohm and 150 mH, respectively. It is fed from a single phase half-controlled rectifier with an a.c. source of 230 volt, 50 Hz. Calculate (i) Motor torque for $\alpha = 60^{\circ}$ and speed = 600 RPM. (ii) motor Speed for $\alpha = 60^{\circ}$ and torque= 20 N-m.	07

- (b) Explain torque and power limitations for combined armature 07 voltage and field control method.
- Q.5 (a) What is meant by input power factor in controlled rectifier? Write 07 the equations.
  - (b) Explain 3-phase full-wave controlled converter. Draw the 07 waveforms of O/P voltage, O/P current and voltage across thyristor1 for  $\alpha$ =30°,  $\alpha$ =90° and  $\alpha$ =120° for continuous conduction.

OR

- Q.5 (a) Explain different types of control strategies for chopper drive. 07
  - (b) Explain the armature control and flux control of dc motors. 07

\*\*\*\*\*