GUJARAT TECHNOLOGICAL UNIVERSITY ME – SEMESTER-1 (NEW) EXAMINATION – WINTER 2016

Subject Code: 2710709Date:06/01/2017Subject Name: Electrical Drives (Power Electronics Group)Time: 2:30 pm to 5:00 pmTime: 2:30 pm to 5:00 pmTotal Marks: 70Instructions:Total Marks: 70

- 1. Attempt all questions.
- 2. Make suitable assumptions wherever necessary.
- 3. Figures to the right indicate full marks.
- Q.1 (a) Derive an expression of steady state stability of an electrical drive. 07
 - (b) Enlist and explain various components of load torques and their significance. 07
- Q.2 (a) Derive an expression for maximum torque of a 3-phase induction motor and 07 justify that it is independent of rotor resistance.
 - (b) Explain various modes for discontinuous conduction of 1-phase fully controlled rectifier-fed separately excited motor for motoring operation for $\alpha < \gamma$. Draw relevant waveforms with usual notations. Also, explain the effects of change in (i) load torque (ii) firing angle α and (iii) angular speed of drive.

OR

- (b) Explain various modes for regenerative braking operation of separately excited motor for $\alpha < \gamma$ and discontinuous conduction of 1-phase rectifier with controlled fly-wheeling. Draw relevant waveforms with usual notations. 07
- **Q.3** (a) A 220V, 1750rpm, 20A separately excited motor is controlled by a 1-phase 07 fully controlled rectifier with an ac source voltage of 230A, 50Hz. Armature resistance and inductance are $R_a = 2.6\Omega$ and $L_a = 28$ mH, respectively.
 - i. What should be the value of the firing angle to get the 75% of rated torque at 1150rpm? Also, Comment on nature of current in regard of continuous or discontinuous.
 - ii. Calculate the firing angle for the rated braking torque and -1500rpm?
 - (b) Explain the significance of current control in electric drive system. Explain 07 various methods of current control with suitable example and block diagram.

OR

- **Q.3** (a) A 220V, 1750rpm, 20A separately excited motor is controlled by a 1-phase 07 fully controlled rectifier with an ac source voltage of 230A, 50Hz. Armature resistance and inductance are $R_a = 2.6\Omega$ and $L_a = 28$ mH, respectively.
 - i. What would be motor torque for $\alpha = 45^{\circ}$ and speed = 475rpm.
 - ii. What would be motor torque for $\alpha = 45^{\circ}$ and speed = 1100rpm.
 - (b) Explain the simultaneous control technique in dual converter to control 07 circulating current of separately excited dc motor. Also, state advantages and disadvantages of it.
- Q.4 (a) Explain the composite braking scheme for chopper based separately excited dc 07 motor. Also, enlist its advantages and disadvantages.
 - (b) Write a brief note on modified Kramer drive. 07

OR

- Q.4 (a) Discuss the method of injection of voltage in the rotor circuit to control the speed 07 of an induction motor in a super-synchronous region.
 - (b) Discuss the operation of a cylindrical rotor synchronous motor operating from a 07 current source.

- Q.5 (a) Explain the use of induction motors in fan and pump drives applications and 07 derive expression for ratio of maximum to rated motor current.
 - (b) A 3-phase, 400 V, 50 Hz,10 kW, 960 rpm, star-connected wound-rotor 07 induction motor has the following parameters: *R_s* = 0.4 Ω, *R_r* ' = 0.6 Ω, *X_s* = *X_r* ' = 2 Ω Stator to rotor turns ratio is 2.5. The speed at full load torque is reduced to 600 rpm by injecting a voltage into the slip rings. Calculate the magnitude and frequency of the injected voltage. Assume the injected voltage is in phase with V.

OR

- Q.5 (a) Derive expression for current ripple for Time Ratio Control in chopper based 07 drive.
 - (b) A 250 V separately excited dc motor has an armature resistance of 2.5 Ω . When driving a load at 600 rpm with constant torque, the armature takes 20 A. This motor is controlled by a chopper circuit with a frequency of 400 Hz and an input voltage of 250 V.
 - (i) What should be the value of the duty ratio if one wishes to reduce the speed from 600 rpm to 400 rpm, with the load torque maintained constant.
 - (ii) What should be the minimum value of the armature inductance, if the maximum armature current ripple expressed as a percentage of the rated current is not to exceed 10%.
