GUJARAT TECHNOLOGICAL UNIVERSITY ME – SEMESTER-1 (NEW) EXAMINATION – WINTER 2016

Subject Code: 2713108 Date: Subject Name: Medical Instrumentation & systems			04/01/2017	
Ti	me: 2 tructio	2:30 pm to 5:00 pm Total Marks: ons: Attempt all questions. Make suitable assumptions wherever necessary.	70	
Q.1	(a) (b)	Give design of I to V converter. How its sensitivity can be modified? Derive gain equation for current amplifiers.	07 07	
Q.2	(a) (b)	 What is input offset voltage? Explain input-error compensation techniques. Give short explanation of following words Gain bandwidth product Slew rate limiting Transient response Input & output impedance 	07 07	
	(b)	OR Design a second-order notch filter with $f_0=60$ Hz and bandwidth 5Hz.	07	
Q.3	(a) (b)	Explain design concepts of multiple feedback band pass filter. Give technical aspects of magnetically isolated isolation amplifier. OR	07 07	
Q.3	(a) (b)	Explain concepts of generalized impedance converters (GIC). Explain model of resistance simulation using a switched capacitor.	07 07	
Q.4	(a) (b)	Write an introductory note on certification criteria for Medical electronic systems. Draw and explain the noise equivalent circuit for the BJT amplifier. OR	07 07	
Q.4	(a) (b)		07 07	
Q.5	(a) (b)	 Draw the circuit of sample & Hold circuit. explain sampling theorem Explain operational principle of Phase-locked loop. Draw phase detector circuit 	07 07	
		2. Draw phase detector circuit OR		
Q.5	(a) (b)	Explain binary-weighted resistor type digital to analog converter (DAC). Write a brief note on electrical safety issues in medical devices.	07 07	
