Seat No.:	Enrolment No.
Scat No	Emonicii No.

GUJARAT TECHNOLOGICAL UNIVERSITY

ME – SEMESTER III (OLD) – EXAMINATION – WINTER-2016

	•	Code: 734502 Date:27/10/202 Name: EMC in Power Electronics	16
Time: 02:30 pm to 05:00 pm Instructions: Total Mark		s: 70	
	1. 2. 3.	Attempt all questions. Make suitable assumptions wherever necessary. Figures to the right indicate full marks.	
Q.1	(a) (b)	Explain the classification of disturbances by transmission mode. Explain the classification of disturbances by frequency.	07 07
Q.2	(a) (b)	Explain basic terms and conducted EMI references with reference to EMI measurement. Write a short note on measuring the interference current.	07 07
	(b)	OR Write a short note on measuring the interference voltage.	07
Q.3	(a) (b)	Draw and explain basic circuit configuration of EMI filter. Write a short note on Damped EMI filter for low current ratings. OR	07 07
Q.3	(a) (b)	Derive the equations of insertion loss of two port network in terms of Z parameters and ABCD parameters. Explain Laplace transform root calculation method.	07 07
Q.4	(a) (b)	Write a note on EMI from rectifier circuits. Explain the filter design method for voltage attenuation.	07 07 07
Q.4	(a) (b)	OR Write a note on EMI from semiconductor. Explain the noise suppression in relay systems.	07 07
Q.5	(a) (b)	Explain HF characteristics of noise filter circuit elements. Briefly explain the EMC tests as per IEC specifications. OR	07 07
Q.5	(a) (b)	Describe in detail about surge protection devices Draw equivalent circuit for determining the capacitive current of noise suppression and explain it with necessary equation	07 07
