Seat No.:	Enrolment No
-----------	--------------

## GUJARAT TECHNOLOGICAL UNIVERSITY M. E. - SEMESTER – II • EXAMINATION – WINTER 2012

Subject code: 1722602 Date: 31-12-2012 Subject Name: CMOS Circuit Design-II Time: 10.30 am - 01.00 pm**Total Marks: 70 Instructions:** 1. Attempt all questions. 2. Make suitable assumptions wherever necessary. 3. Figures to the right indicate full marks. (a) Discuss Low-noise op-amps using MOSFETs. 07 Q.1**(b)** Discuss Analog Multiplier. 07 Q.2 (a) Discuss the Channel charge injection and clock feedthrough in MOSFET 07 during switching operation. (b) Explain the preamplification stage of comparator circuit. 07 (b) How would you increase the gain bandwidth product of the conventional op-07 amp? Explain your approach in detail. 07 0.3(a) Explain Switched capacitor integrator. Explain PTAT current generation. 07 OR 0.3 (a) Discuss any two application of PLL. 07 (b) Explain supply independent biasing. 07 (a) What are the different issues to be considered in design of sense amplifier? **07** 0.4 Draw basic sense amplifier circuit and discuss its working. **(b)** Discuss buffered opamps using MOSFETs. **07** 0.4 (a) Explain the mechanism of erasing and writing data into flash memory. Draw 07 circuit diagram for a 4-bit NAND flash memory cell and provide the table indicating levels of input signals for erase, program, and read operations. **(b) 07** Explain the working of basic charge pump PLL. **Q.5** (a) Classify ADC and discuss Successive Approximation ADC in brief. 07 **(b)** Discuss Applications of the Schmitt Trigger. **07** OR **Q.5** Classify DAC and discuss current scaling DACs. 07 **(b)** Explain all Multivibrator circuits. 07

\*\*\*\*\*