(b)

Enrolment No.

GUJARAT TECHNOLOGICAL UNIVERSITY M. E. - SEMESTER – I • EXAMINATION – WINTER 2012

Subject code: 710702N Subject Name: Advanced Power Electronics Time: 02.30 pm – 05.00 pm Instructions:

Total Marks: 70

07

Date: 09-01-2013

- 1. Attempt all questions.
- 2. Make suitable assumptions wherever necessary.
- **3.** Figures to the right indicate full marks.
- 4. Support your answer with necessary circuit diagram and waveforms, if required.

Q.1 (a) Compare GTO, IGBT and power BJT.

- i. What is the need of isolation in driver circuit? Discuss the basic two 07 ways of isolating gate signal.
 - ii. Discuss salient features of IGBT.
- Q.2 (a) What are the limitations of the single stage conversion in Switching mode 07 regulators? Explain the working of Buck regulators with the help of circuit diagram and various waveforms.
 - (b) Derive the expressions for the peak to peak ripple current, peak to peak 07 capacitor voltage and critical values of inductor and capacitor for continuous mode in a Buck-Boost regulator.

OR

- (b) A Boost regulator has an input voltage of 5 V. The average output voltage is 07 15 V and average load current is 0.5 A. The switching frequency is 25 kHz. If inductor is 150 μ H and Capacitor is 225 μ F, determine (i) duty cycle, (ii) ripple current of inductor, ripple voltage of filter capacitor and (iii) Critical values of L and C for continuous mode.
- Q.3 (a) Compare 120° and 180° modes of firing schemes in a 3-phase inverter. 07 Discuss any one in details with the help of necessary diagram and waveforms.
 - (b) Discuss single pulse and multi-pulse width modulations to reduce harmonics 07 in a 1-phase inverter. Also derive the expression to eliminate a particular harmonic in single pulse width modulation.

OR

- Q.3 (a) Compare voltage source inverter and current source inverter.
 - (b) Discuss the transformer connections to eliminate (i) a particular harmonic 07 and (ii) any two harmonics simultaneously in a 1-phase inverter with the support of necessary waveforms and equations.
- Q.4 (a) Derive the expression for the r.m.s. output voltage of a 3-phase, 3-wire star 07 connected AC controller with resistive load. Also draw the necessary circuit and waveforms for firing angle of 60° .
 - (b) In a 3-phase full wave AC star connected voltage regulator has the following 07 data:

Input r.m.s. voltage (line to line) = 210 V, 50 Hz, firing angle $\alpha = \frac{\pi}{3}$ and load resistance R_L = 10 ohm. Determine output r.m.s. voltage and power factor.

07

- Q.4 (a) Compare cycloconverter and dc link converter. Describe 3-phase to 3-phase 07 cycloconverter with relevant circuit using 18 thyristors.
- Q.4 (b) Explain the basic principle of operation of a cycloconverter with a neat 07 circuit diagram. Prove that the fundamental r.m.s. value of per phase output voltage of low frequency for an m-pulse cycloconverter is given by Eor = Eph $\left(\frac{m}{n}\right) sin \left(\frac{m}{n}\right)$.
- Q.5 (a) With the help of block diagram explain the basic principle of operation of 07 SMPS.
 - (b) A 3-phase to 1-phase cycloconverter employs three pulse positive and 07 negative group converters. Each converter is supplied from delta/star transformer with per phase turns ratio of 3:1. The supply voltage is 410 V, 50 Hz. The load has resistance of 4 ohm and at low output frequency, the inductive reactance is 3 ohm. The commutation overlap and thyristor turn-off time limit the firing in the inversion mode to 160⁰. Calculate: (i) the r.m.s. output voltage, (ii) r.m.s. output current and (iii) output power.

OR

- Q.5 (a) State the main requirements and advantages of a good current transformer. 07 Also state different types of core materials.
 - (b) Discuss the salient features of transformer and dc inductor design for an ac- 07 dc converter.
