Seat No.:		Enrolment No			
		GUJARAT TECHNOLOGICAL UNIVERSI	GUJARAT TECHNOLOGICAL UNIVERSITY		
		M. E SEMESTER – I • EXAMINATION – WINTER 201			
Subj	ect o	code: 712907N Date: 1	0/01/2013		
Subj	ect I	Name: Power Devices & Applications			
Time	: 02	2.30 pm - 05.00 pm Total M	Iarks: 70		
Instr	uct	tions:			
		Attempt all questions.			
		Make suitable assumptions wherever necessary.			
	3.	Figures to the right indicate full marks.			
Q.1	(a)	List out & explain Various types of Power Converters.		06	
V.1	(b)	• • • • • • • • • • • • • • • • • • • •	fier.	03	
	(c)	•		05	
Q.2	(a)			07	
		2. A diode has a reverse recovery time of 2.5µs. If di/dt is 17.5 A	$A/\mu s$, find a		
	(b)	stored charge & peak reverse current. Compare Various types of firing circuits.		07	
	(D)	OR		U/	
	(b)		derive the	07	
	` ′	equation for Periodic time T of UJT relaxation oscillator.			
Q.3	(a)	<u> </u>	ary diagram	07	
	(b)	& design consideration. What are the adventages of PUT? Design PUT 30 minute time de	lov oirouit	07	
	(b)	What are the advantages of PUT? Design PUT-30 minute time de OR	iay circuit.	U/	
Q.3	(a)		uit using a	07	
	()	thyristor having a dv/dt rating of 20 V/µs, the source inductance	_		
		The rms value of supply voltage is 230V. If the damping factor is	s 0.75, find		
		out the value of R and C of the snubber circuit.			
	(b)	Compare SUS and SBS in tabular forms.		07	
Q.4	(a)	Describe different region of operation of a thyristor with the help	of	07	
V. 7	(a)	V-I characteristics.	OI .	U1	
	(b)		ons of UPS	07	
	` '	systems.			
		OR			
Q.4	(a)	•	ote on Gate	07	
	(b)	characteristics of SCR.	nimanit	07	
	(b)	Why battery charging needed? Draw & explain battery charging of	circuit.	07	
Q.5	(a)	Write a detailed note on Light-dimmer control.		07	
C	(b)	_		07	
		turn on a power transistor is given by (VI/6) T joules where	_		
		voltage, I= on state current and T is turn on time. Assume voltage	e & current		
		to be linear.			
Q.5	(a)	OR Explain power circuit of ideal zero voltage switch with neat sketc	h	07	
V.2	(a) (b)			07	

characteristics of IGBT with neat sketches.