## GUJARAT TECHNOLOGICAL UNIVERSITY M. E. - SEMESTER – I • EXAMINATION – WINTER 2012

Subject code: 714404NDate: 16-01-2013Subject Name: VLSI in Wireless communication systems (Major elective-1)Time: 02.30 pm - 05.00 pmTotal Marks: 70Instructions:			
	1. A 2. N	Attempt all questions. Make suitable assumptions wherever necessary. Figures to the right indicate full marks.	
Q.1	(a)	Explain the operation of BPSK modulator and demodulator with necessary block diagram also derive the necessary equations for the same	07
	(b)		07
Q.2	(a)	Explain the operation of Gilbert Mixer in details with necessary circuit diagram along with design steps for the same.	07
	(b)		07
Q.3	(a)	Draw heterodyne architecture of RF receiver and also explain the functions of Band selection filter, Image rejection filter and channel filter	07
	(b)	Draw input bias scheme for Wideband LNA & explain	07
Q.4	(a)	Discuss for receiver design, the effects of non idealities into the	07
	(b)	corresponding design parameters. Draw generalized LNA topology and its equivalent lumped parameter of an amplifier and explain its working	07
Q.5	(a) (b)	Compare Wideband versus Narrow band analog to digital converters Explain the phase detector based on EXOR gate using CMOS technology	07 07
Q. 6	(a) (b)	Explain the multipath fading in details Describe the operation of charge pump with necessary generic model	07 07
Q. 7	(a)	Draw the circuit employed to match the load with signal source in an LNA	07
	(b)	and derive the expression for Zin and comment on it. Explain PLL based frequency synthesizer with necessary block diagram	07

\*\*\*\*\*\*