Seat No.:	Enrolment No.

GUJARAT TECHNOLOGICAL UNIVERSITY

M. E. - SEMESTER – I • EXAMINATION – WINTER 2012

•	•	code: 714502N Date: 09-01-2013	
		Name: Solid State DC Drives	
		2.30 pm – 05.00 pm Total Marks: 70	
Inst		tions:	
	2.	Attempt all questions. Make suitable assumptions wherever necessary. Figures to the right indicate full marks.	
Q.1	(a)	What are the main factors which decide the choice of DC drive for a given application?	07
	(b)	State essential parts of DC drives. What is the current status of DC drives?	07
Q.2	(a)	For type-A dc chopper with RLE load and continuous load current condition, show that the per unit ripple current is maximum when duty cycle is 0.5. Also draw the necessary waveforms and circuit diagram.	07
	(b)		07
	(b)		07
Q.3	(a)	What factors limit the maximum speeds of field controlled DC motors? A 230 V, 1000 rpm, 105 A separately excited dc motor has an armature resistance of 0.06 ohm. Calculate the value of flux as a percent of rated flux for motor speed of 1500 rpm when load is such that the developed motor	07
	(b)	power is maintained constant at rated value for all speeds above rated speed. State and explain the important features of various braking methods of dc motors. OR	07
Q.3	(a)		07
	(1.)	voltage control is employed for getting speeds less than rated. Why?	
	(b)	Explain why a dc series motor is more suited to deal with torque over loads than other dc motors.	07
Q.4	(a)		07
	(b)	series motor. Why torque becomes zero at finite speed? A 230 V, 870 rpm, 100 A separately excited dc motor has an armature resistance of 0.05 ohm. It is coupled to an overhauling load with a torque of 400 N-m. Determine the speed at which motor can hold the load by regenerative braking. OR	07
Q.4	(a) (b)	State and explain the disadvantages of using a motor of wrong rating. What are the reasons for using load equalization in an electrical drive? Why current sensing is required in electrical drives? What are the common	07 07

- Q.5 (a) How does a phase locked loop speed control scheme operate? Where do you 07 use it?
 - (b) A constant speed drive has duty cycle (i) Load rising from 0 to 400 kW: 5 min. (ii) Uniform load of 500 kW: 5 min (iii) Regenerative power of 400 kW returned to the supply: 4 min. (iv) Remains idle for: 2 min. Estimate power rating of the motor. Assume losses to be proportional to (power)².

OR

- Q.5 (a) Describe relative merits and demerits of four quadrant dc drives employing 07 non-circulating and circulating current dual converters.
 - (b) A fully controlled rectifier-fed separately excited dc motor is required to operate in motoring and braking operations in the forward direction. Only one fully controlled rectifier is available. What switching arrangement will be required? Explain.
