

GUJARAT TECHNOLOGICAL UNIVERSITY**M. E. - SEMESTER – II • EXAMINATION – WINTER • 2013****Subject code: 1720302****Date: 27-12-2013****Subject Name: Advance Instrumentation****Time: 10.30 am – 01.00 pm****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Figures to the right indicate full marks.
3. Make suitable assumptions wherever necessary and mention it clearly in your solution.
4. Consider design parameters of 741 opamp when not mentioned explicitly in question.
5. Necessary circuit diagrams are must while deriving for equations.
6. Show all node voltages and branch currents used in your derivations.

Q.1 Derive the equation of feedback factor β for the circuit in figure 1 if $r_d = 2 \text{ M}\Omega$ and $r_o = 75 \text{ }\Omega$. Justify whether it is positive feedback circuit or negative feedback circuit. **14**

Q.2 (a) Find the gain of the circuit in figure 2 known as dual op-amp instrumentation amplifier with variable gain. Consider virtual short condition. **07**

(b) Illustrate slew rate with necessary waveforms and derivations. An opamp shown in figure 3 has an input bias current of $20 \text{ }\mu\text{A}$ and a compensation capacitance C_c of 30 pF , and slew rate of $0.633 \text{ V}/\mu\text{s}$, find its response $v_o(t)$ to a step input of -0.5 V . Consider $R_1 = 3 \text{ K}\Omega$ and $R_2 = 12 \text{ K}\Omega$. **07**

OR

(b) Explain frequency compensation using loop-gain reduction method with the help of necessary diagrams and equations. **07**

Q.3 Draw the circuit diagram of strain-gauge bridge, having four strain-gauges, connected with instrumentation amplifier (IA), referred to as a load cell, and having calibration facility to account for gauge resistances and reference voltage tolerances. **14**

(i) Derive the relationship of output voltage with gain of IA, reference voltage, and fractional change in resistance δ .

(ii) Let the strain-gauges be of 100Ω , $\pm 1 \%$ types and their maximum power dissipation limited to 20 mW to avoid excessive self heating. Assume that $V_{\text{REF}} = 10 \text{ V} \pm 5\%$, specify suitable values for R_1 through R_4 used for calibration.

(iii) Outline the calibration procedure.

OR

Q.3 Draw the circuit diagram of single op-amp bridge amplifier having transducer connected to only one arm of the bridge. **14**

(i) Derive the relationship of output voltage with fractional change in resistance δ . What is the disadvantage of this bridge?

(ii) Let the transducer Pt. RTD having a temperature coefficient of $0.00392/^\circ\text{C}$ is connected to one arm of the bridge and let $V_{\text{REF}} = 10 \text{ V}$. Specify values for resistors and gain A suitable for achieving an output sensitivity of $0.15 \text{ V}/^\circ\text{C}$ near 0°C . To avoid self heating in the RTD, limit its power dissipation to less than 0.15 mW .

(iii) Compute output voltage at 100 °C.

- Q.4 (a)** Draw the circuit diagrams of Howland and Improved Howland circuits and prove the advantage of Improved Howland circuit over Howland circuit by suitable example. **07**
- (b)** Explain the effect of finite gain bandwidth product on integrator circuits with the help of diagrams and equations. **07**

OR

- Q.4** Derive the equations of A_{dm} , A_{cm} , and $CMRR_{dB}$ for difference amplifier shown in figure 4. If the resistance $R_1 = 1.01 \text{ K}\Omega$, $R_2 = 99.7 \text{ K}\Omega$, $R_3 = 0.995 \text{ K}\Omega$, $R_4 = 102 \text{ K}\Omega$, estimate A_{dm} , A_{cm} , and $CMRR_{dB}$. **14**

- Q.5 (a)** Draw the circuit diagram of second order high-pass KRC filter and derive equations for dc gain, ω_0 , and Q . Design a filter with $f_0 = 500 \text{ Hz}$ and $Q = 2$ using unity gain circuit. **07**
- (b)** For the circuit diagram shown in figure 5 derive the equation to find output dc noise voltage. Suggest a way to reduce this noise voltage. Justify your suggestion. If $R_1 = 33 \text{ K}\Omega$, $R_2 = 3.3 \text{ M}\Omega$, op amp input bias current of 80 nA and input offset current of 20 nA then calculate output dc noise voltage when (i) $R_p = 0$ and (ii) $R_p = R_1 \parallel R_2$. **07**

OR

- Q.5 (a)** Draw the circuit diagram of second order band-pass KRC filter and derive equations for dc gain, and ω_0 . Design a filter with $f_0 = 1000 \text{ Hz}$ and bandwidth of 200 Hz. What is its resonance gain? **07**
- (b)** The difference amplifier of figure 6 uses a 741 opamp having $CMRR$ of 90dB and perfectly matched resistances $R_1 = 15 \text{ K}\Omega$ and $R_2 = 150 \text{ K}\Omega$. If the inputs are tied together and driven with a common signal v_i (i.e $v_1 = v_2 = v_i$) then estimate the typical change in v_o if (i) v_i is slowly changed from 0 to 10V and (ii) v_i is a 10 KHz, 10 V peak to peak sine wave. Consider $CMRR$ at 10 KHz of 57 dB. **07**

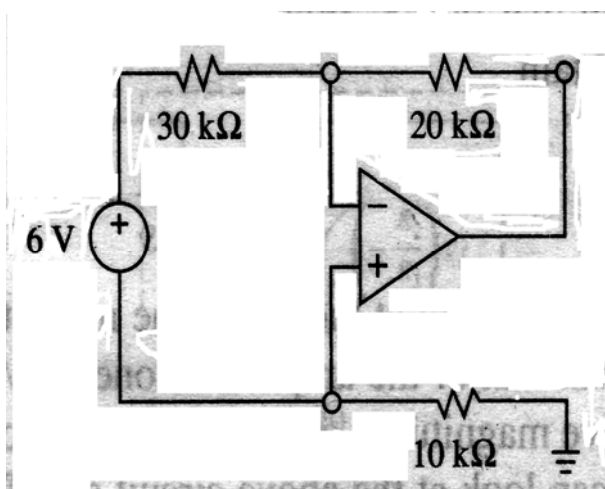


Figure-1

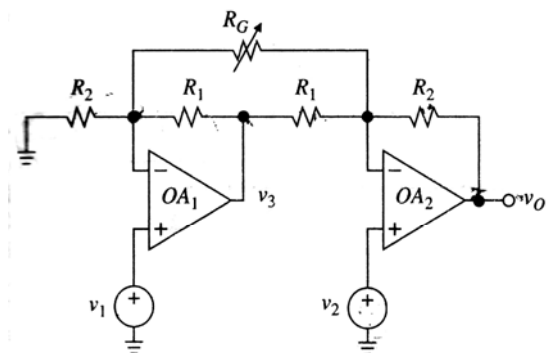


Figure-2

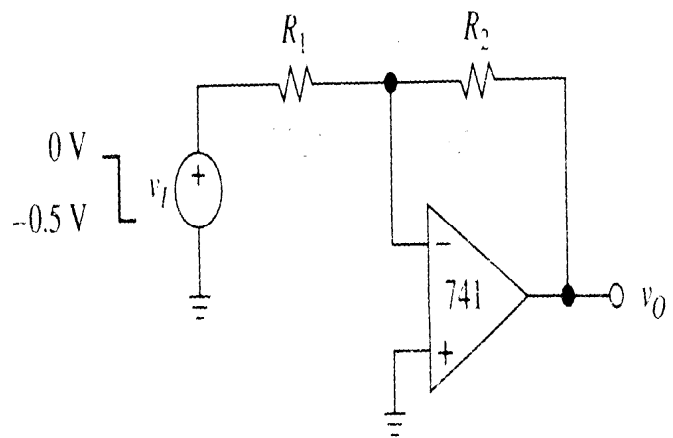


Figure-3

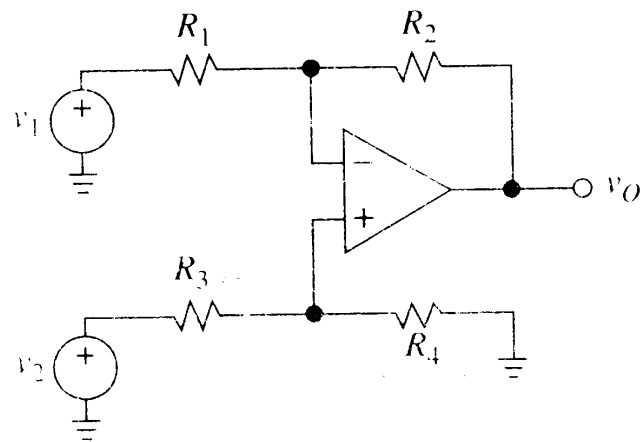


Figure-4

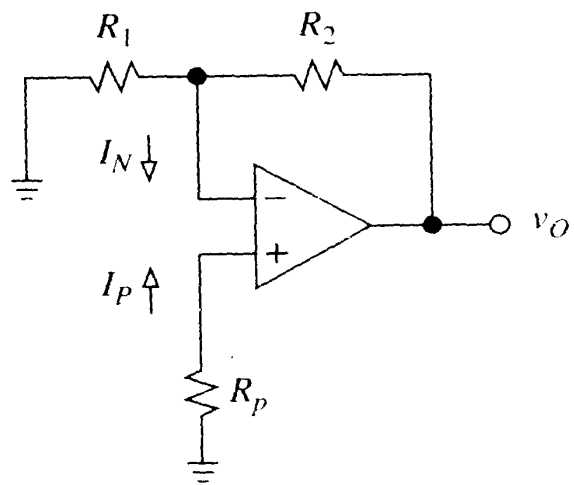


Figure-5

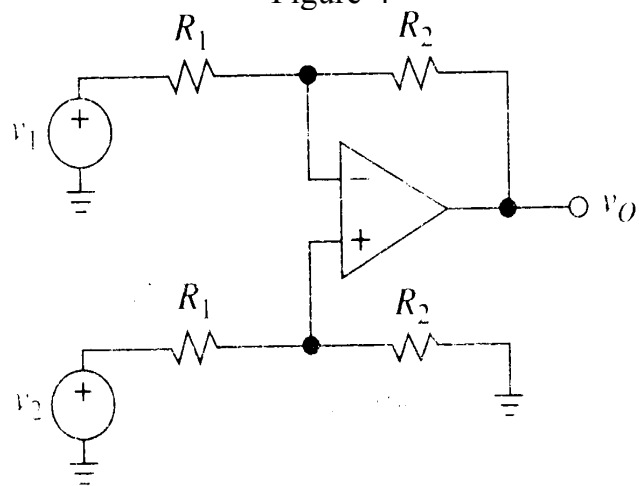


Figure-6