

GUJARAT TECHNOLOGICAL UNIVERSITY
M. E. - SEMESTER – I • EXAMINATION – WINTER • 2013

Subject code: 712907N**Date: 30-12-2013****Subject Name: Power Devices & Applications****Time: 10.30 am – 01.00 pm****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

- Q.1 (a)** Explain V-I characteristics of Power BJT in various operating regions. 07
 Enlist various differences between Power BJT and Signal BJT.
- (b)** An SCR has V_g-I_g characteristics given as $V_g = 1.5 + 8I_g$. In a certain application, the gate voltage consists of rectangular pulses of 12V and of duration $50\mu s$ with 20% duty cycle. Determine the value of series resistor (R_g) in gate circuit to limit the peak power dissipation in the gate to 5W. Also calculate average power dissipation in the gate. 07
- Q.2 (a)** Explain the basic structure of an IGBT and briefly explain its principle of operation with neat diagram. 07
- (b)** Explain the construction and the V-I characteristics of a PUT. 07
- OR**
- (b)** Explain the application of PUT to trigger an SCR. 07
- Q.3 (a)** Explain Class-A commutation of SCR with necessary waveforms. Also enlist its drawbacks. 07
- (b)** Briefly explain the various turn on methods for SCR. Which method is preferable? Justify. 07
- OR**
- Q.3 (a)** Explain two-transistor equivalent model of SCR. Also derive the equation for the anode current. 07
- (b)** Explain di/dt and dv/dt protection circuits. 07
- Q.4 (a)** Compare SCR, Power BJT, Power MOSFET and IGBT in a tabular form. 07
- (b)** A Class-C commutation circuit has both the resistances are of 10Ω , commutation capacitor is of $5\mu F$ and supply voltage is 200V. Turn OFF time of both the SCRs is $50\mu s$. Make necessary calculations and state whether the circuit components are correct for satisfactory commutation of SCRs. If not then suggest the solution. 07
- OR**
- Q.4 (a)** Explain power circuit of ideal zero voltage switch with neat diagram and necessary waveform. 07
- (b)** Why battery charging is needed? Draw and explain battery charging circuit. 07
- Q.5 (a)** Enlist the applications of UPS. What is the meaning of Online UPS and Offline UPS? Explain any one of them with neat block diagram. 07
- (b)** Compare R, RC and UJT firing circuits in tabular form. What is the major technical drawback of R triggering circuit? Why? 07
- OR**
- Q.5 (a)** Explain the working principle of a 1-phase light dimmer with power saving 07

feature. Also derive the RMS output voltage equation.

- (b) How SUS differs from SBS? Draw their circuit symbols. Explain any one of them with neat diagram. **07**
