Enrolment No._____

GUJARAT TECHNOLOGICAL UNIVERSITY M. E. - SEMESTER – I • EXAMINATION – WINTER • 2013

Subject code: 714404NDate: 06-01-2014Subject Name: VLSI in Wireless communication systemsTime: 10.30 am – 01.00 pmTotal Marks: 70Instructions:1. Attempt all questions.2. Make suitable assumptions wherever necessary.3. Figures to the right indicate full mark.			
Q.1	(a)	Explain the operation of QPSK modulator and demodulator with necessary block diagram also derive the necessary equations for the same	07
	(b)	Define noise figure and also for noisy two port networks of K- stages, each with noise, derive equation for Noise figure	07
Q.2	(a)	Define the types of mixers and explain the operation of Gilbert Mixer in details with necessary circuit diagram along with design steps for the same.	07
	(b)	Explain the design step of sigma delta modulator in detail OR	07
	(b)	Draw heterodyne architecture of RF receiver and also explain the functions of Band selection filter, Image rejection filter and channel filter	07
Q.3	(a)	Discuss for receiver design, the effects of non idealities into the corresponding	07
	(b)	design parameters. Draw generalized LNA topology and its equivalent lumped parameter of an amplifier and explain its working OR	07
Q.3	(a) (b)	Compare Wideband versus Narrow band analog to digital converters Explain the phase detector based on EXOR gate using CMOS technology	07 07
Q. 4	(a) (b)	Explain the multipath fading in details Describe the operation of charge pump with necessary generic model	07 07
Q. 4		OR Draw the circuit employed to match the load with signal source in an LNA and	07
Q. 4	(a)	derive the expression for Zin and comment on it. Explain PLL based frequency synthesizer with necessary block diagram	07
0.5	(b)		07
Q-5	(a)	Draw input bias scheme for Wideband LNA & explain	
	(b)	Compare wideband LNA and Narrow band LNA OR	07
Q-5	(a) (b)	Explain switch capacitor based 1-bit analog to digital converter Explain the operations of FSK modulator and demodulator with block diagrams.	07 07
