Seat N	.:			Enrolment No	
			GUJARAT TECHNOLOGICAL UNIVERSITY M. E SEMESTER – I • EXAMINATION – WINTER • 2013		
Subje	ect	cod	le: 715403N Date: 03-01-2014	4	
_			me: Electronic System Design		
Time	: 1	0.30	0 am - 01.00 pm Total Marks: 70		
Instr	uc	tio	ıs:		
	1.	At	tempt all questions.		
			ake suitable assumptions wherever necessary.		
	3.	Fig	gures to the right indicate full marks.		
Q.1		(a)	inverting mode with two resistors. Obtain expressions of their voltage	07	
		(1.)	gain.	07	
		(b)	Explain the following parameters of OP-AMP: (i) Slew rate	07	
			(ii) Common Mode Rejection Ratio		
			(iii) Power Supply rejection Ratio		
			(iv) Input Offset Voltage		
Q.2		(a)	Explain the following methods of D/A conversion:	07	
			(i) Parallel method		
			(ii) Weighting method		
		(b)	(iii) Counter method Draw the circuit diagram of a full wave bridge rectifier. Obtain the	07	
		(b)	expression of average and rms value of load voltage for resistive load. OR	U7	
		(b)	Explain the successive approximation A/D converter.	07	
		` /	11		
Q.3		(a)	Draw the basic circuit diagram of a BiCMOS inverter with resistive	07	
		.	load. Discuss the switching delay in BiCMOS logic circuits.		
		(b)	Write a short note on BiCMOS applications.	07	
Q.3		(a)	OR Write short notes on:	07	
Ų.J		(a)	(i) Controllability and Observability	U/	

inverter. **Q.4**

07

07

- Write short notes on:
 - (i) Scan-Based Techniques
 - (ii) Buil-In Self Test Techniques

(ii) Ad Hoc testable Design Techniques

(b) Consider a CMOS inverter circuit with the following parameters:

(b) Obtain the expressions of V_{OH} , V_{OL} , V_{IL} and V_{IH} of a resistive load CMOS 07

 $V_{DD} = 3.3 \text{ V}$

$$\begin{split} V_{DD} &= 5.3 \text{ V} \\ V_{TO,n} &= 0.6 \text{ V} \\ V_{TO,p} &= -0.7 \text{ V} \\ K_n &= 200 \text{ } \mu \text{ A} / \text{V}^2 \\ K_p &= 80 \text{ } \mu \text{ A} / \text{V}^2 \\ K_R &= 2.5 \end{split}$$

Calculate the noise margins of the circuit.

OR

Q.4	(a)	Draw the models for Electro Static Discharge testing. Also draw a typical ESD protection network circuit.	07
	(b)	Write a short note on Electromagnetic Compatibilty.	07
Q.5	(a)	Obtain the expression of switching power dissipation of CMOS inverter.	07
	(b)	Discuss the issues related to grounding of Electronic Systems in brief. OR	07
Q.5	(a)	Draw the typical circuit diagrams of a typical active low pass, high pass and band pass filters.	07
	(b)	Enlist the important packaging concerns of Electronic circuits. Explain the following package types: DIP,PGA,CCP,QFP,MCM	07
