Seat 1	No.: _	Enrolment No.	_
		GUJARAT TECHNOLOGICAL UNIVERSITY	
		M. E SEMESTER - II • EXAMINATION - WINTER • 2014	
Subj	ect c	ode: 1720705 Date: 04-12-2014	
Subj	ect N	Name: Application of Power Electronics in Power System	
Time	e: 02	:30 pm - 05:00 pm Total Marks: 70	
Inst	ructi	ions:	
	1.	Attempt all questions.	
		Make suitable assumptions wherever necessary.	
0.4		Figures to the right indicate full marks.	^=
Q.1	(a)	Explain conventional control mechanism in ac power system.	07 07
	(b)	Explain single phase TCR. Draw the waveforms for current through TCR, voltage across thyristor and voltage across inductor for firing angle = 105°	U /
		and $= 150^{\circ}$.	
Q.2	(a)	with $l = 0.85$ mH/km, $c = 14.5$ nF/km mid-point compensated line, the mid	07
		point voltage V_{mc} is to be held at 1.05 p.u., the realistic mid-point VAR compensator, rated to operate from -1000 to +1000 MVAR. Find the working operating range for mid-point voltage and operating load angle .	
	<i>(</i> 1.)	Also comment on result.	^=
	(b)	Define and explain following in brief.	07
		a) SVC b) FACTS controller c) UPFC d) IPFC OR	
	(b)	Draw and explain STATCOM and each block of its control system.	07
Q.3	(a)	Explain the basic principle of TCSC. Also explain different modes of TCSC	07
	<i>a</i> >	operation.	0.5
	(b)	Explain TCSC constant-angle (CA) controller model in detail. Also draw the block diagram of CA controller with PI regulator. OR	07
Q.3	(a)	Explain the basic concepts of NGH-SSR damping scheme.	07
	(b)	Explain the V-I and X-I capability characteristics of the single module TCSC for continuous time application, short duration implementation and 1-10s.	07
Q.4	(a)	Discuss the 12-pulse TCR and derive the TCR in 12-pulse arrangement with	07
	4)	which maximum numbers of harmonics are cancelled.	0.5
	(b)	Draw and explain the V-I characteristics of STATCOM. OR	07
Q.4	(a)	Draw and explain the block diagram of a typical TCSC power control	07
	(b)	structure. Compare STATCOM and SVC as FACTS devices.	07
0.5	(b)	-	
Q.5	(a)	Derive the expression for mid-point voltage of a symmetrical transmission line as a function of power flow.	07
	(b)	List different analytical methods used for SSR analysis. State advantages and	07
	, ,	disadvantages of one of them. Also draw and explain the IEEE First	
		Benchmark System with STATCOM for SSR damping.	
0.5	(2)	OR White the energting principle of UDEC and also list its applications	0.5
Q.5	(a) (b)	Write the operating principle of UPFC and also list its applications. Prove that the net Var rating of the series compensator is much less than that	07 07
	(0)	required of a shunt compensator for the same change in power transfer.	U /
