Seat No.: _____

Enrolment No.____

Seat No.:		Enrolment No.	
GUJARAT TECHNOLOGICAL UNIVERSITY M. E SEMESTER – II • EXAMINATION – WINTER • 2014 Subject code:1722901 Date: 02-12-2014 Subject Name: Advanced Power Converters & Control			
Time: 02:30 pm - 05:00 pm Total Marks: 70 Instructions:			
1. 2.	Att Ma	tempt all questions. The suitable assumptions wherever necessary. Sures to the right indicate full marks.	
Q.1	(a) (b)		07 07
Q.2	(a) (b)	Discuss current mode control of DC-DC converter. Explain transformer connections of 18-pulse converters. Compare it with 6- pulse converter. OR	07 07
	(b)		07
Q.3	(a) (b)	Give the comparison between all three configurations of multilevel inverter. Explain operation of ZCS converter with diagram and wave forms. OR	07 07
Q.3	(a) (b)	Explain the H bridge topology of three level MLI with switching table. Discuss working principle of parallel inverter. Give its application area.	07 07
Q.4	(a) (b)	Discuss commutation and protection issues related to matrix converters. Explain control characteristics of converters used in HVDC transmission system.	07 07
Q.4	(a) (b)	OR Discuss bidirectional switch topologies for matrix converter. Explain comparator based control for rectifier system.	07 07
Q.5	(a) (b)	Compare AC and DC transmission lines. And discuss HVDC transmission. Discuss pulse width modulation technique for matrix converter.	07 07
Q.5	(a) (b)	Discuss voltage mode control of DC-DC converters in closed loop. Explain averaging model of DC-DC converter with appropriate example.	07 07
