Seat No.: Enrolment No			
		GUJARAT TECHNOLOGICAL UNIVERSITY	
		M. E SEMESTER – II • EXAMINATION – WINTER • 2014	
S	ubje	ct code: 1724502 Date: 03-12-2014	
	-	ct Name: Power Electronics-II	
	_	02:30 pm - 05:00 pm Total Marks: 70	
		etions:	
		1. Attempt all questions.	
		2. Make suitable assumptions wherever necessary.	
		3. Figures to the right indicate full marks.	
0.1	(.)	Final in the hards are marked for some and a final in	0.5
Q.1	(a) (b)	Explain the basic concepts of series resonance circuit.  What is power factor? Derive its formula for Linear load.	07 07
	(D)	what is power factor? Derive its formula for Linear load.	U /
Q.2	(a)	List the application of multilevel inverter and explain one in detail.	07
	(b)	Explain the Frequency response of series resonant inverter.	07
		OR	
	<b>(b)</b>	What are the modifications required in basic series resonant inverter? Explain any	07
		one.	
0.3	( )		0.5
Q.3	(a)	What is the main function of resonant switch converter? Explain ZCS resonant	07
	(b)	converter.  Explain switching state in 7-level H-bridge inverter.	07
	(0)	OR	U /
Q.3	(a)	Explain the diode clamped 5-level inverter	07
Q.D	(b)	A Thyristor based series resonant inverter has following parameters:	07
	(0)	R = 1 $\acute{a}$ , L = 0.1 mH, C = 10 $\mu$ F, $t_q$ = 12 $\mu$ Sec.	U /
		Find the maximum switching frequency for non overlap operation of inverter.	
		The the manner of terms and the man of the production of an investor.	
Q.4	(a)	A series resonant inverter with bidirectional switches in half bridge topology has	07
	` ′	following circuit parameters:	
		(1) $C_1 = C_2 = 4 \mu F$ , (2) $L_r = 40 \mu H$ , (3) $R = 2 \text{ á}$ ,	
		(4) $E_{dc} = 120 \text{ Volt and (5) } t_q = 20 \mu \text{Sec.}$	
		Assume output frequency to be 40% of resonant frequency.	
		Determine: (a) Resonant frequency,	
		<ul><li>(b) Max. operating frequency,</li><li>(c) Time required by current to reach at peak value,</li></ul>	
		(d) Peak device current.	
	(b)	Define: (1) Voltage distortion factor, (2) Current distortion factor and (3)	07
	(0)	Displacement factor. Give relation between these three factors and power factor for	0,
		non linear load.	
		OR	
Q.4	(a)	Explain boost converter based power factor control topology.	07
	<b>(b)</b>	With the help of block diagram explain the principle of active power filter.	07
Q.5	(a)	What is the meaning of multipulse converter? Give its advantages and explain	07
	(I-)	working of six pulse converter.	0.5
	<b>(b)</b>	Explain AC voltage PWM controller with waveforms.  OR	07
Q.5	(a)	Discus the steps to design inductor for boost dc-dc converter.	07
V.2	(a) (b)	Discuss the steps to design high frequency transformer.	07
	(0)	**************************************	<i>U 1</i>