Seat No.:	Enrolment No.
-----------	---------------

GUJARAT TECHNOLOGICAL UNIVERSITY M. E. - SEMESTER – I • EXAMINATION – WINTER • 2014

Subject code: 2713108 Date: 07-01-2015 **Subject Name: Medical Instrumentation and Systems** Time: 02:30 pm - 05:00 pm **Total Marks: 70 Instructions:** 1. Attempt all questions. Make suitable assumptions wherever necessary. 3. Figures to the right indicate full marks. Q.1 Design current to voltage converters. How sensitivity of I to V converter can **07** (a) be improve? **07** Derive equation of gain for instrumentation amplifier and why it is preferable **(b)** for biomedical applications? Q.207 Give short note on various Electrical safety issues in medical devices. (a) Draw circuit of KRC low pass filter and Derive equation of Gain. **07 (b)** Find the equivalent impedance of a Generalized impedance converter toward (b) 07 ground. Draw circuits of Inductor simulator and D element realization. Q.3 Explain designing of Switched capacitor filters. 07 (a) Give description about transient response of OPAMP. 07 (b) OR Derive the equation of errors caused by input bias and offset current in op-Q.3(a) **07 (b)** Derive the equation of errors caused by input offset voltage and thermal drift 07 in op-amp. **Q.4** (a) Design 4 bit switched current source type DAC. Range of output voltage is 0 **07** to 5 volt. Explain working of R-2R ladder type DAC. (b) 07 OR Design 3 bit flash type Analog to Digital converter for analog input 0 to 8 0.4 07 (a) volt. Explain two-noise source model for a noisy amplikers **(b) 07 Q.5** Draw and explain the noise equivalent circuit for the BJT ampliker. 07 (a) What is the need of isolation amplifier in body parameter acquisition? And 07 **(b)** explain any one type of medical isolation. OR **Q.5** Explain architecture of phase lock loop and their biomedical application. 07 (a) Explain balanced bridge diode type and electro mechanical chopper phase 07 (b) sensitive type phase sensitive rectifier circuits.
