Seat No.:	
No	

GUJARAT TECHNOLOGICAL UNIVERSITY M. E. - SEMESTER – I • EXAMINATION – WINTER • 2014

Subject code: 710702N Date: 02-12-2014

Subject Name: Advanced Power Electronics

Time: 10:30 am - 01:00 pm Total Marks: 70

Instructions:

1. Attempt all questions.

2. Make suitable assumptions wherever necessary.

3. Figures to the right indicate full marks.

Q.1	(a)	Compare Power MOSFET, IGBT and SCR with respect to their construction, ratings available, switching characteristics, switching speeds, applications etc.	
	(b)	Draw the circuit diagram of boost converter and explain the continuous conduction mode of operation with necessary waveform and equation.	07
Q.2	(a)	With neat circuit diagram and waveforms, explain the working of forward converter. Derive output voltage in terms of duty ratio.	07
	(b)	Draw circuit diagram of cuk converter and explain its working with waveform and equations.	07
	(1)	OR	0=
	(b)	Describe the necessity of Isolation of gate and base drives and explain how they are implemented using the pulse transformer and optoisolator with necessary circuit diagrams.	07
Q.3	(a)	Explain the working of three phase bridge inverter in 150° conduction mode with necessary waveforms.	07
	(b)	Explain various harmonic reduction techniques used in inverter.	07
		OR	
Q.3	(a)	Explain space vector control of 3-phase bridge inverter. Show that the amplitude of output voltage with space vector technique is 15.5 % higher than that obtained with sine-triangle PWM technique.	07
	(b)	Explain unipolar modulation in relation to inverter operation. How is it different from bi-polar modulation? What is the effect of these two schemes on the output voltage's harmonic spectrum?	07
Q.4	(a)	Explain the working of three-phase current source inverter with neat diagram and necessary waveforms. Compare it with voltage source inverter.	07
	(b)	Explain three phase bidirectional delta connected controller with wave form of gate pulse & line current for $\alpha = 120^{\circ}$.	07
		OR	
Q.4	(a)	Classify A.C. voltage controller & explain principle of ON-OFF control & Phase angle control.	07
	(b)	Explain the working of three phase full wave A.C. controller for $\alpha = 60^{\circ}$ with the wave forms of Input line voltage, Input phase voltage, Gate pulse for each Thyristor and Output phase voltage.	07
Q.5	(a)	Describe the high frequency transformer design for fly back converter with it's topology and waveforms.	07
	(b)	Write a brief note on the design criteria to be considered in the design of SMPS.	07
		OR	

Q.5	(a)	How design of magnetic components used in power electronic circuit is	07
		different than when used in normal electric circuits? Explain 'Area of Product'	
		method in brief.	
	(b)	Explain the operation of three-phase to single phase cycloconverter with neat	07
		diagram and necessary waveform. Derive the expression of output voltage.	
