Enrolment

GUJARAT TECHNOLOGICAL UNIVERSITY M. E. - SEMESTER – I • EXAMINATION – WINTER • 2014

Subject code: 713101N Subject Name: Medical System Design Time: 10:30 am - 01:00 pm Instructions:

Date: 01-12-2014

Total Marks: 70

- - Attempt all questions.
 Make suitable assumptions wherever necessary.
 - 3. Figures to the right indicate full marks.

| (a) (b) | Design 15V/2A regulated power supply with fold back current protection circuit. Where, $V_{in}=230 \pm 20\%$, $I_{pri}=190$ mA. (Assume Ripple Voltage: 10% of V_o) Sketch Necessary Voltage Wave form at every stage of Above Power supply design. | 10 04 |
|------------|--|--|
| (a) (b) | Enlist ideal Operation Amplifier Characteristics. Explain Constant current limiting circuit with necessary safe operating area. OR | 07 07 |
| (b) | Explain fold back current limiting circuit with necessary safe operating area. | 07 |
| (a) (b) | Explain Current –Voltage Converters. Explain Instrumentation Amplifier with its advantages. OR | 07 07 |
| (a) (b) | Explain Voltage-Current Converters. Derive Equation for V_{CM} and V_{DM} for Difference Amplifier. | 07 07 |
| (a) (b) | Explain Op-amp as a Voltage Comparator with any one application in detail. A type OP27 op-amp has the following specifications. Large signal voltage gain= 8 x10 ⁵ , CMRR= 94db, SVRR=86db, e_{na} = 3nv/Hz, Input Noise Current I_{na} = 0.4pA/Hz, f_{ci} =140Hz. Compute the AC errors of the amplifier in the frequency band 1Hz to 333Hz. Calculate the n bit accuracy for the full scale output voltage of 10V AC(peak to peak) | 07 07 |
| | OR | |
| (a) (b) | Derive the equation for ΔV_T for Non Inverting Schmitt Trigger. Explain sample and Hold Circuit & determine acquisition time to 0.1% full scale or a 10V step input with C _H = 10nf and R _{ON =} 300Ω. | 07 07 |
| (a) (b) | Explain PLL and explain its operation in Locked Condition. Explain 4-bit approximation A to D converter. OR | 07 07 |
| (a) (b) | Explain Logarithmic Characteristic and transdiode configuration of amplifier. Write a short note on Pipe Line structured ADC. | 07 07 |
| | (b) (a) (b) (c) (c) | circuit. Where, V_{in}=230 ±20%, I_{pri} =190mA. (Assume Ripple Voltage: 10% of V_o) (b) Sketch Necessary Voltage Wave form at every stage of Above Power supply design. (a) Enlist ideal Operation Amplifier Characteristics. (b) Explain Constant current limiting circuit with necessary safe operating area. OR (b) Explain fold back current limiting circuit with necessary safe operating area. (a) Explain fold back current limiting circuit with necessary safe operating area. (a) Explain fold back current limiting circuit with necessary safe operating area. (a) Explain fold back current limiting circuit with necessary safe operating area. (a) Explain Voltage-Current Converters. (b) Explain Noltage-Current Converters. (c) Derive Equation for V_{CM} and V_{DM} for Difference Amplifier. (a) Explain Op-amp as a Voltage Comparator with any one application in detail. (b) A type OP27 op-amp has the following specifications. Large signal voltage gain= 8 x10⁵, CMRR= 94db, SVRR=86db, e_{na}= 3nv/Hz, Input Noise Current I_{na}= 0.4pA/Hz, f_{ci} =140Hz. Compute the AC errors of the amplifier in the frequency band 1Hz to 333Hz. Calculate the n bit accuracy for the full scale output voltage of 10V AC(peak to peak) OR (a) Derive the equation for ΔV_T for Non Inverting Schmitt Trigger. (b) Explain sample and Hold Circuit & determine acquisition time to 0.1% full scale or a 10V step input with C_H= 10nf and R_{ON=} 300Ω. (a) Explain 4-bit approximation A to D converter. OR (a) Explain Logarithmic Characteristic and transdiode configuration of amplifier. |
