| Seat No.: | Enrolment No. |
|-----------|---------------|
|           |               |

## GUJARAT TECHNOLOGICAL UNIVERSITY M. E. - SEMESTER - I • EXAMINATION - WINTER • 2014

Subject code: 714502N Date: 02-12-2014 **Subject Name: Solid State DC Drives** Time: 10:30 am - 01:00 pm **Total Marks: 70 Instructions:** 1. Attempt all questions. 2. Make suitable assumptions wherever necessary. 3. Figures to the right indicate full marks. 0.1 Find the equivalent moment of inertia and equivalent torque of motor load 07 system referred to shaft with rotational and translation motion. (b) State and explain various braking methods of dc motors. 07 Q.2Explain the Ward Leonard speed control method of DC motor. 07 (a) Explain the armature control and flux control of dc motors and also explain (b) 07 constant torque and constant power operation. A 220V, 875rpm, 150A Separately excited dc motor has an armature resistance 07 of 0.06á. It is fed from a single phase fully controlled rectifier with ac voltage of 220V, 50Hz. Assuming continuous conduction, calculate (1) Firing angle for rated torque and 750 rpm. (2) Motor speed for = 160 degree and rated torque. 0.3 Draw circuit diagram, waveform and write the equations for 1-phase half **07** (a) controlled bridge converter separately excited dc motor drive where current of the armature is assumed to be discontinuous. A 200 V, 10.5 A, 1000 rpm shunt motor has the armature and field resistance 07 of 0.5 and 400 respectively. It drives a load whose torque is constant at rated motor torque. Calculate motor speed if the source voltage drop to 175 V. 0.3 Give and Explain simulation block diagram of speed control of DC motor with **07** current control loop and current limiting. Explain with block diagram the control of circulating current in dual converter 07 with simultaneous control **Q.4** (a) Develop a transfer function of separately excited DC motor with speed control **07** (b) Explain class C type chopper control DC motor drive. 07 OR 0.4 Explain comparison of P, PI, and PID controller. 07 (a) Draw circuit diagram, waveform and write the equations for 3-phase full **07** controlled rectifier control of separately excited dc motor. **Q.5** Explain synchronizing firing of circuit, pulse transformer and draw circuit for **07** (a) gate protection. (b) Explain different types of control strategies for chopper drive. **07** OR **Q.5** Draw the basic block diagram of electric drive system and explain each block. 07 (a) Explain Phase Locked Loop (PLL) Control of DC Drives. **07** (b) \*\*\*\*\*