

GUJARAT TECHNOLOGICAL UNIVERSITY

P.D.D.C. Sem - IV Examination June- 2011

Subject code: X41103

Subject Name: Integrated Circuits and Applications

Date:06/06/2011

Time: 10.30 am – 01.30 pm

Total Marks: 70

Instructions:

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

- Q.1** (a) What are the problems associated with basic differentiator circuit? How they can be eliminated? Justify the answer with the help of circuit diagrams and frequency response. **07**
- (b) Draw and explain triangular wave generator circuit and its waveform. **07**

- Q.2** (a) Draw and explain block diagram representation of typical op-amp. **07**
- (b) Explain following electrical parameters of op-amp in brief: **07**
1. Input offset voltage
 2. Input bias current
 3. common-mode rejection ratio
 4. Supply voltage rejection ratio

OR

- (b) Draw voltage series feedback amplifier circuit and derive expressions for the following: **07**
1. Closed loop voltage gain
 2. Input resistance with feedback
 3. Bandwidth with feedback

- Q.3** (a) Draw and explain offset voltage compensated noninverting and differential amplifiers. **07**
- (b) Draw differential instrumentation amplifier using a transducer bridge and derive expression for its gain. **07**

OR

- Q.3** (a) Draw and explain second order low pass Butterworth filter and its frequency response. Give design steps for this filter. **07**
- (b) What are the problems associated with zero crossing detector circuit. Draw and explain the circuit which solves these problems. **07**

- Q.4** (a) Design a first order high-pass filter at a cutoff frequency of 1 KHz with a passband gain of 2. Plot the frequency response of the same. **07**
- (b) Draw and explain active narrow band reject filter and its frequency response. Design 60 Hz active notch filter. **07**

OR

- Q.4** (a) What is the application of sample and hold circuit? Draw and explain the working of sample and hold circuit. **07**
- (b) Draw and explain positive and negative clipper circuits. **07**

- Q.5** (a) Explain the operation of 555 IC as a monostable multivibrator with necessary schematic diagram and waveforms. **07**
- (b) Explain adjustable positive voltage regulators. **07**

OR

- Q.5** (a) What are the features of Sallen-key filters? Draw second order low pass and band pass Sallen-key filters. **07**
- (b) Discuss the application of Phase Locked Loop as frequency multiplier. **07**
