Enrolment No.\_\_\_\_

## **GUJARAT TECHNOLOGICAL UNIVERSITY**

PDDC - SEMESTER-I - EXAMINATION – SUMMER 2017 Subject Code: X11101 Date:01/06/2017

Subject Name: BASIC ELECTRONICS

Time: 02:30 PM to 05:00 PM

Instructions:

- 1. Attempt any five questions.
- 2. Make suitable assumptions wherever necessary.
- 3. Figures to the right indicate full marks.
- **Q.1** (a) Define following terms:
  - 1. Mobility
  - 2. Barrier Potential
  - 3. Dark Current of Photodiode
  - 4. Tunneling effect
  - 5. Transition capacitance
  - 6. Thermal runaway
  - 7. Pinch-off voltage of JFET
  - (b) Justify semiconductor behaves as an insulator as well metal. Explain the energy band diagram of Insulator, Semiconductor and Metal with necessary diagrams.
- Q.2 (a) State the law of mass action. List and explain the electrical properties of Si and O7 Ge with necessary information.
  - (b) Explain the temperature dependency of V-I characteristics of diode. Justify reverse leakage current doubles in every 10 °C rise in temperature.
- Q.3 (a) List the different types of clipping circuit and explain biased clipper in detail.
  (b) Draw and explain the full wave bridge rectifier with necessary circuit and
  07
  - (b) Draw and explain the full wave bridge rectifier with necessary circuit and 07 waveforms. Derive the value for  $E_{dc}$  for it.
- Q.4 (a) Explain the current components in transistor with necessary diagrams.
   (b) Why transistor operated in active region for amplification? Explain the CE 07 amplifier with output characteristics showing the different region of operation.
- Q.5 (a) What do you mean by Hybrid-parameters? How it can be useful for analyzing 07 transistor? Draw the equivalent h-parameter circuit for CB and CC configuration.
  - (b) Explain Miller's theorem and its dual with necessary circuit diagrams. 07
- Q.6 (a) What is biasing? Explain the self-bias circuit with necessary derivations.
  (b) Draw the construction of JFET and explain its working with its V-I characteristics.
  07 Give the comparison between BJT and FET.
- Q.7 (a) Explain the working of transformer coupled audio power amplifier with 07 necessary circuit diagrams.
  - (b) What is cross-over distortion? Explain the complementary push pull amplifier 07 with necessary circuit diagrams.

\*\*\*\*\*

07

**Total Marks: 70**