## GUJARAT TECHNOLOGICAL UNIVERSITY

PDDC- SEMESTER-II - EXAMINATION - SUMMER 2017

Subject Code: X20901 Date:30/05/2017

**Subject Name: CIRCUITS AND NETWORKS** 


Time: 10:30 AM to 01:00 PM Total Marks: 70

**Instructions:** 

- 1. Attempt any five questions.
- 2. Make suitable assumptions wherever necessary.
- 3. Figures to the right indicate full marks.
- Q.1 (a) Discuss the following.

07

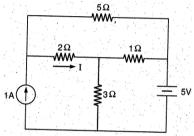- 1) Linear and Non Linear Element
- 2) Active and Passive network.2) Unileteral and Pileteral network
- 3) Unilateral and Bilateral network.
- (b) Find the current passing through the  $2\Omega$  resistor using Mesh analysis for the circuit shown in the figure.




Q.2 (a) Explain the following.

**Q.5** 

07

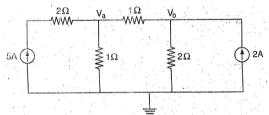
- 1) Tree 2) junction 3) loop 4) Cut set 5) link 6) Ideal Source 7) Co tree
- (b) Using the nodal voltage analysis, find the current in all resistors for the network shown in figure.



- Q.3 (a) Derive the condition for a maximum power transfer 07
  - **(b)** Discuss the techniques of Source transformation.

07

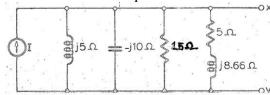- Q.4 (a) Derive the initial and final value theorem of Laplace transform.
- 07
- (b) Discuss initial conditions in basic elements of network(a) Derive formulae to convert given 'Y' parameters into 'h' parameters
- 07
- (a) Derive formulae to convert given 'Y' parameters into 'h' parameters.
   (b) I = 33 ∠-13 amp then find thevenin's equivalent circuit across x-y.
- 07 07



**Q.6** (a) State and explain Super position theorem.

07 07

(b) The open circuit impedance parameters of a two port network are  $Z_{11} = 5\Omega$ ,  $Z_{12} = 3\Omega$ ,  $Z_{21} = 3\Omega$ ,  $Z_{22} = 4\Omega$ . Determine ABCD parameters. Also check network is reciprocal and symmetrical or not.

State and explain Thevenin's theorem.

Write down fundamental loop matrix and Incidence matrix for given figure. **(b)** 

