GUJARAT TECHNOLOGICAL UNIVERSITY

| PDDC- SEMESTER-II - EXAMINATION – SUMMER 2017 | | | |
|---|------------|--|-----------|
| Subject Code: X20902 Date:01/00 | | | 17 |
| Subject Name: ELECTRICAL MEASUREMENT I & II | | | |
| Time: 10:30 AM to 01:00 PM Total Marl | | | 70 |
| Ins | | ons: Attempt any five questions. Make suitable assumptions wherever necessary. Figures to the right indicate full marks. | |
| Q.1 | (a) (b) | Define the terms: (1) Sensitivity (2) Resolution (3) Accuracy (4) Precision (5) Error (6) Calibration (7) Dead zone Explain the construction and working of a single phase energy meter. | 07 07 |
| Q.2 | (a) (b) | Explain the construction and working of attraction type moving iron instrument. Explain the construction and working of megger. Write its applications. | 07 07 |
| Q.3 | (a) (b) | Explain two wattmeter method of three phase power measurement with neat sketch. Explain Wheatstone bridge for measurement of low resistance. | 07 07 |
| Q.4 | (a) (b) | Discuss with neat diagram the DC potentiometer-Crompton Potentiometer with its calibration and test procedure. Discuss the different methods of damping in indicating instruments. | 07 07 |
| Q.5 | (a) (b) | Explain the construction and working of PMMC type voltmeter. State the different methods of measuring medium resistances. Explain any one method in detail | 07 07 |
| Q.6 | (a) (b) | Explain measurement of Capacitance by any A.C. bridge. Explain Maxwell's bridge for measurement of self inductance. | 07 07 |
| Q.7 | (a) (b) | Explain various effects with which deflecting torque is produced? Draw the equivalent circuit and phasor diagram of a current transformer. Derive the expression for ratio and phase angle errors. | 07 07 |
