Seat No.:	Enrolment No.

## **GUJARAT TECHNOLOGICAL UNIVERSITY**

PDDC- SEMESTER-III - EXAMINATION - SUMMER 2017

Subject Code: X30902 Date:29/05/2017 **Subject Name: Analog & Digital Electronics** Time: 02:30 PM to 05:00 PM **Total Marks: 70 Instructions:** 1. Attempt all questions. 2. Make suitable assumptions wherever necessary. 3. Figures to the right indicate full marks. What is an op-amp? Explain how is op-amp used as voltage follower. **07** 0.1 (a) What are the specifications of ideal op-amp? Discuss the following parameters 07 **(b)** of op-amp (i) Slew rate (ii) CMRR (iii) Virtual ground. **Q.2** (a) Do as directed: (i)  $(110.111)_2 = ($ (ii)  $(1001)_8 = ($ 07  $)_{10}$ (iv)  $(100111111)_2 = ($ (iii)  $(A6F.CD)_{16} = ($ )8 )16 **(b)** State and prove De Morgan's theorem with examples. **07** OR Simplify the Boolean function:  $\mathbf{F} = \overline{\mathbf{A}} \, \overline{\mathbf{B}} \, \overline{\mathbf{C}} + \mathbf{A} \overline{\mathbf{C}} \, \overline{\mathbf{D}} + \mathbf{A} \overline{\mathbf{B}} + \mathbf{A} \mathbf{B} \mathbf{C} \overline{\mathbf{D}} + \overline{\mathbf{A}} \, \overline{\mathbf{B}} \, \mathbf{C}$ **07 (b)** (i) Express it in sum of minterms. (ii) Find the minimal sum of products using K-map. 0.3 Simplify the following logic expressions using Boolean algebra: (a)  $A + \overline{A}B$ **07** (a) (b) (A + B)(B + C)(C + A) (c)  $(A + B)(\overline{A} + C)$ Explain briefly the operation of 4 to 1 line multiplexer with diagram. 07 **(b)** OR 0.3 (a) Explain TTL circuit in detail. 07 Explain full-adder with logic circuit and truth table. **(b)** 07 0.4 Draw the block diagram of IC 555 and explain its operation in detail. 07 (a) What is a flip flop? Explain briefly S-R flip-flop with truth table. **(b)** 07 OR Explain the Synchronous counter. 0.4 (a) 07 Explain the J-K flip-flop with logic diagram and truth table. 07 **(b)** Do as directed: (i) Encode (2345)<sub>10</sub> in BCD. (ii) Encode (1236)<sub>10</sub> in excess-3 **Q.5** 07 (a) code. (iii) Find 1's and 2's complement of number 10100111. Draw symbols and truth table for AND, OR, NOT gates. Prove that NAND and **07 (b)** NOR gates are universal gates. OR **Q.5** What is zero-crossing detector? Explain operation of zero-crossing detector 07 (a) with circuit. Explain the operation of Schmitt trigger circuit. **(b) 07** \*\*\*\*\*