

GUJARAT TECHNOLOGICAL UNIVERSITY**PDDC- SEMESTER-IV - EXAMINATION – SUMMER 2017****Subject Code: X41103****Date: 31/05/2017****Subject Name: Integrated Circuits and Applications****Time: 10:30 AM TO 01:00 PM****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

Q.1 (a) Draw and explain block diagram of typical op-amp. Also draw equivalent circuit of it. **07**

(b) Define following terms with respect to op-amp **07**

- 1) ICMR 2) CMRR 3) Slew Rate 4) PSSR
- 5) Bandwidth 6) Input offset voltage 7) Input bias current.


Q.2 (a) Define negative feedback. List types of feedback and explain voltage series feedback. **07**

(b) Draw and explain differential amplifier using one op-amp. **07**

OR

(b) Draw and explain peaking amplifier using op-amp. **07**

Q.3 (a) **07**

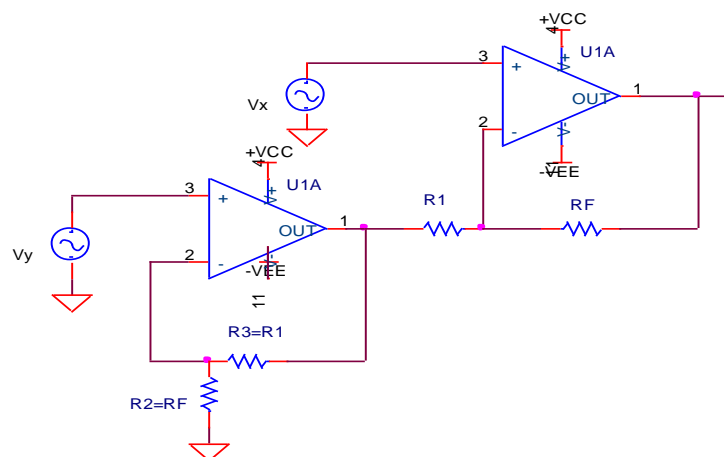


The following specifications are given for differential amplifier of figure shown above. $R_1 = R_3 = 680 \text{ ohm}$, $R_F = R_2 = 6.8 \text{ k}\Omega$, $V_x = -1.5 \text{ Vpp}$, and $V_y = -2 \text{ Vpp}$ sine waves at 1 kHz . The op-amp is 741C. Calculate

- (a) voltage gain and i/p resistance and
- (b) o/p voltage of amplifier. Assume o/p is initially nulled ($V_{o0T} = 0 \text{ V}$).

(b) Explain opamp as summing amplifier. **07**

OR

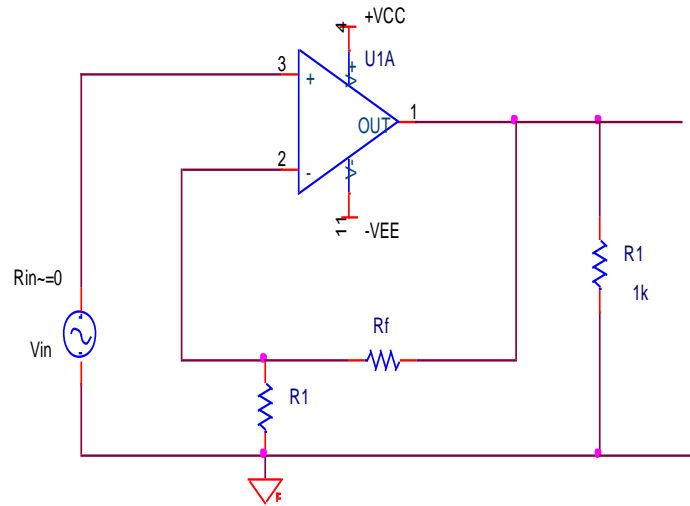

741C op-amp having following parameters is connected as non-inverting amplifier, as shown in above figure, with $R_1=1\text{ K}\Omega$ and $R_F=10\text{ K}\Omega$:

$A=200,000$, $R_i=2\text{ M}\Omega$, $R_o=75\text{ }\Omega$, $f_o\cong 5\text{ Hz}$, Supply voltage = $\pm 15\text{ V}$

Output voltage swing = $\pm 13\text{ V}$.

Compute values of A_F , R_{iF} , R_{oF} , f_F and V_{oot} .

- (b) Explain op-amp as differentiator with necessary figures.

07

- Q.4** (a) Draw sample and hold circuit diagram using op-amp. Also explain working of it.

07

- (b) Draw Schmitt trigger circuit diagram using op-amp. Also explain working of it.

07

OR

- Q.4** (a) Draw triangular and saw-toothed waveform generator circuit diagram using op-amp. Also explain working of it.

07

- (b) Explain classifications of filters. Draw Butterworth Low pass filter circuit diagram.

07

- Q.5** (a) Explain Block diagram of 555 timer IC. List applications of it.

07

- (b) Explain running ramp generator using op-amp.

07

OR

- Q.5** (a) Draw Block diagram of PLL and explain it.

07

- (b) Explain Voltage regulators. List different types of it. Also list application of it.

07
