Seat No.:	Enrolment No.

GUJARAT TECHNOLOGICAL UNIVERSITY PDDC - SEMESTER-III • EXAMINATION – SUMMER 2013

Subject Code: X 30901 Date: 09-05-2013 **Subject Name: Basic Electronics** Time: 02.30 pm - 05.00 pm **Total Marks: 70 Instructions:** 1. Attempt all questions. 2. Make suitable assumptions wherever necessary. 3. Figures to the right indicate full marks. Q.1 (a) Explain energy band diagram of insulator, semiconductor and metal. 07 **(b)** Explain formation of n type and p type semiconductors. 07 **Q.2** Explain Drift current and Diffusion current. **07** (a) **(b)** Explain mobility and conductivity. Also derive equation of each. 07 OR **(b)** Explain Hall effect in detail. 07 **Q.3** (a) What is transition capacitance? Derive equation for it. 07 Explain forward and reverse biasing of diode. 07 **Q.3** (a) Draw and explain the Volt-ampere characteristic of a PN junction diode. **07 (b)** Explain zener diode as a voltage regulator. 07 (a) Draw the circuit diagram explain the working of a full wave rectifier with 07 0.4 necessary waveforms. (b) Explain the working of transistor in CE configuration. Also draw its input-output 07 characteristics. OR 07 **Q.4** (a) Explain PN junction as a rectifier. (b) Compare CB, CE and CC transistor configurations. Which is the widely used **07** configuration? Why. 0.5 State different biasing techniques used fir biasing transistor amplifiers, Explain **07** any one in detailed. 07 **(b)** Explain construction and working of n- channel JFET. OR **Q.5** (a) Explain in details : (1) Thermal runaway (2) Stability factor. 07 Classify the power amplifiers based on position of Q point, Operating cycle and 07 efficiency.
