Seat No.:	Enrolment No.
-----------	---------------

GUJARAT TECHNOLOGICAL UNIVERSITY PDDC - SEMESTER-III • EXAMINATION – SUMMER 2013

Subject Code: V 30002

Date: 13.05.2013

	•	Coue. A 50702 Date. 15-05-2015	
	-	Name: Analog and Digital Electronics	
		2.30 pm - 05.00 pm Total Marks: 70	
Instr	uction		
	2.	Attempt all questions. Make suitable assumptions wherever necessary. Figures to the right indicate full marks.	
Q.1	(a) (b)	Draw and Explain the use of op-amp as a Schmitt trigger. Sketch the circuit of Op-amp as Integrator and explain with necessary waveforms.	07 07
Q.2	(a) (b)	Explain ideal Inverting & Non-inverting amplifier. Draw Block Diagram of an Op-amp. Explain Function of each block. OR	07 07
	(b)	List and discuss characteristics of an ideal Op-amp.	07
Q.3	(a)	Sketch the diagram of 555 timers as a Monostable Multivibrator. Explain its working and derive equation for frequency of output waveform.	07
	(b)	Classify IC Voltage regulators. Explain Basic three terminal IC regulators with the help of Block diagram.	07
		OR	
Q.3	(a)	Prove that NOR and NAND gates are universal.	07
	(b)	State & Explain De'Morgan's 1st & 2nd Law.	07
Q.4	(a)	What do you mean by a K map? List its advantages and disadvantages.	07
	(b)	Describe J K flip flop. How J-K flip-flop differ from S-R flip-flop? OR	07
Q.4	(a)	Explain operations of S-R flip flop with the help of logic symbol, circuit diagram and truth table.	07
	(b)	Classify Shift registers. Explain Serial In Parallel Out and Parallel In Parallel Out shift register.	07
Q.5	(a)	What is Decoder? Explain 3 to 8 decoder circuit using truth table and logic diagram.	07
	(b)	Explain Weighted Resistor type DAC converter OR	07
Q.5	(a)	List the various logic families available and explain in brief the specifications of Digital IC'S.	07
	(b)	Derive Full Adder with necessary truth table & K-Map. Also express it with AOI logic diagram.	07
