GUJARAT TECHNOLOGICAL UNIVERSITY PDDC - SEMESTER-IV • EXAMINATION – SUMMER 2013

Subject Code: X41103 Date: 10-06-2013		
Su Ti	ubject Name: Integrated Circuits and Applications ime: 10.30 am - 01.00 pm Total Marks: 70 structions:	
 Attempt all questions. Make suitable assumptions wherever necessary. 		
Q.1	 3. Figures to the right indicate full marks. (a) Explain peaking amplifier using op-amp in detail (b) Explain voltage to current converter with floating load using op-amp with application as diode match finder 	07 07
Q.2	 (a) Explain differential input and differential output amplifier using op-amp in detail (b) Explain voltage follower and current to voltage converter using op-amp OR 	07 07
	(b) Explain instrumentation amplifier using transducer bridge and op-amp	07
Q.3	 (a) Explain integrator using op-amp in detail (b) 1) Design a differentiator to differentiate an input signal that varies in frequency from 10 Hz to about 1 kHz 2) If a sine wave of 1V peak at 1000 Hz is applied to the differentiator of part (1), draw its output waveform. 	07 07
	OR	
Q.3	 (a) Explain differentiator using op-amp in detail (b) The 741C op-amp having the following parameters is connected as a noninverting amplifier, as shown fig: 1, with R₁ = 1kΩ and R_F = 10 kΩ: A=200000, R_i=2MΩ, R₀=75Ω, f₀≃5Hz, supply voltages=∓15V, and output voltage swing=∓13V. Compute the values of A_F, R_{iF}, R₀_F, f_F, and V₀₀T 	07 07
Q.4	 (a) Explain operation of 555 Timer as an astable multivibrator (b) Explain Schmitt trigger in detail 	07 07
Q.4	(a) Explain triangular wave generator using op-amp in detail(b) Explain absolute-value output circuit using op-amp in detail	07 07
Q.5	 (a) Explain biquad circuit in detail (b) Explain operating principle of phase locked loop OR 	07 07
Q.5		07 07
	$\begin{array}{c} V_{1} \\ P_{in} \equiv 0.0 \\ V_{id} \\ V_{2} \\ V_{3} \\ V_{4} \\ V_{2} \\ V_{2} \\ V_{2} \\ V_{3} \\ V_{4} \\ V_{2} \\ V_{4} \\ V_{2} \\ V_{4} \\ V_{5} \\$	
