		abject Code: X11101 Date: 21-06-2014 abject Name: Basic Electronics	
	Ti	ime: 02:30 pm - 05:00 pm Total Marks: 70 structions:	
		<ol> <li>Attempt all questions.</li> <li>Make suitable assumptions wherever necessary.</li> <li>Figures to the right indicate full marks.</li> </ol>	
Q.1	(a)	<ol> <li>State Pauli's exclusion principle.</li> <li>What is cut-in voltage?         Write approximate value of cut-in voltage for silicon and germanium diode.</li> <li>Define volt-equivalent of temperature.</li> <li>Define peak-inverse-voltage.</li> <li>Define Barrier Potential.</li> <li>What is electron volt? Define ev unit of energy.</li> <li>What is mean life time of a carrier?</li> </ol>	07
	<b>(b)</b>		07
Q.2	(a) (b)	Explain mobility and conductivity using electron-gas theory. Also derive the expression for current density.	07 07
	<b>(b)</b>	OR  Explain energy band diagram of insulators, semiconductor and conductor. Explain the electrical properties of germanium and silicon	07
Q.3	(a)	Draw the circuit diagram of full wave bridge rectifier and give its input and output waveforms. Also derive the expression for the dc current.	<b>07</b>
	(b)	A bar of n-type silicon has length of 10 cm and circular cross section area of 20 mm <sup>2</sup> . When it is subjected to a voltage of 4 volt along its length, the current flowing through it is 10 mA. Calculate the concentration of free electrons and drift velocity of electrons. Assume mobility of free electrons to be 1300 cm <sup>2</sup> /v-s.	07
Q.3	(a)	OR  Draw following diode circuits with input and output waveforms.	07
<u></u>	()	<ol> <li>Voltage doubler circuit</li> <li>Positive clipping circuit.</li> <li>Positive clamper circuit.</li> </ol>	- ·
	(b)	<u> </u>	07
Q.4	(a)	Draw the circuit of CE configuration of transistor. Explain input and output characteristics. Derive $\alpha = \beta/\beta + 1$ .	07
	<b>(b)</b>	Determine the h-parameter for the two port network. Draw the hybrid model for CE,	<b>07</b>

OR

GUJARAT TECHNOLOGICAL UNIVERSITY PDDC - SEMESTER-I • EXAMINATION - SUMMER • 2014

Seat No.: \_\_\_\_\_

CB and CC configuration.

Enrolment No.\_\_\_\_

- Q.4 (a) Explain the h-parameter model of CE amplifier with Bypass resistor  $R_E$  and derive the expression for  $A_i, A_v, R_i$  and  $R_o$ 
  - (b) What is biasing? Why biasing is required for transistor? List biasing methods for 07 transistor. Draw and explain the circuit of voltage divider biasing.
- Q.5 (a) Give constructional details of JFET and give its characteristics. Why FET is called **07** voltage controlled device?
  - (b) Classify the power amplifier based on the position of Q-point on the ac load line. Also 07 explain class-B push-pull amplifier.

## OR

- Q.5 (a) State the role of voltage regulators in power supplies? Discuss working of a series 07 voltage regulator.
  - (b) Explain the operation of Emitter follower amplifier. Why it is named as emitter 07 follower.

\*\*\*\*\*