GUJARAT TECHNOLOGICAL UNIVERSITY PDDC - SEMESTER-II • EXAMINATION – SUMMER • 2014

Subject Code: X20901 Date: 20-0			6-2014	
Subject Name: Circuit and Network Time: 10:30 am – 01:00 pm Total Marks Instructions:			s: 70	
	1. 2.	Attempt any 5 questions. Make suitable assumptions wherever necessary. Figures to the right indicate full marks.		
Q.1	(a)	 Define following terms clearly: (1) Linear network (2) Lumped parameter (3) Dependant source (4) Duality (5) Bilateral network (6) Passive circuit elements (7) Active circuit elements 	07	
	(b)		07	
Q.2	(a) (b)	Explain various source transformation techniques. Determine currents through all voltage sources using nodal analysis (The circuit is shown in fig 1)	07 07	
	(b)		07	
Q.3	(a) (b)		07 07	
Q.3	(a)	OR	07	
Q.5	(a) (b)		07 07	
Q.4	(a) (b)	Discuss applications of Laplace transformation in network analysis.	07 07	
		values of <i>i</i> , di/dt and d^2i/dt^2 at $t=0_+$. OR		
Q.4	(a) (b)	Discuss concept of poles and zeros in a network function.	07 07	
Q.5	(a) (b)	Find Z parameters for the circuit shown in fig. 5. What is incidence matrix? How it can be formed? Discuss its properties.	07 07	
Q.5	(a)	OR Find transmission parameters for the circuit shown in fig. 5.	07	
2.0	(b)		07	













