GUJARAT TECHNOLOGICAL UNIVERSITY PDDC - SEMESTER-III • EXAMINATION – SUMMER • 2014

Subject Code: X 30901Date: 18-06-20Subject Name: Basic ElectronicsTotal Marks: 'Time: 02:30 pm - 05:00 pmTotal Marks: '			014	
)		
11150		Attempt all questions. Make suitable assumptions wherever necessary. Figures to the right indicate full marks.		
Q.1	(a) (b)	Explain (1) Charged Particle (2) Field Intensity (3) Potential Energy. State and explain electrical properties of Ge and Si.	07 07	
Q.2	(a) (b)	Explain the energy band theory of crystals, insulators, semiconductors and metals with necessary diagrams. What is the stability factor? Derive its equation against the change in I_{CO} , V_{BE} , and β .	07 07	
	(b)	OR Explain "open–circuited p-n junction" and "p-n junction as a rectifier" with necessary diagrams.	07	
Q.3	(a) (b)	Explain h-parameter for CE configurations. Write technical note on tunnel diode. OR	07 07	
Q.3	(a) (b)	Explain push-pull amplifier with necessary diagrams. Write technical note on photovoltaic effect.	07 07	
Q.4	(a) (b)	Explain piecewise linear diode model. Discuss "clipping at two independent levels" with suitable circuit diagram and their wave forms.	07 07	
Q.4	(a)	OR Explain transformer coupled audio power amplifier in detail.	07	
Ľ	(b)	What is the necessity of filter? Explain capacitor filter in detail.	07	
Q.5	(a) (b)	Explain the transistor as an amplifier with necessary diagrams. Give comparison of CB, CE and CC configuration of transistor amplifier. OR	07 07	
Q.5	(a)	What is load line analysis for transistor amplifier? In which condition the position of operating point is shifting?	07	
	(b)	Explain what is pinch off voltage? Discuss V-I characteristic of FET.	07	
