Enrolment No._____

GUJARAT TECHNOLOGICAL UNIVERSITY PDDC - SEMESTER-VIII • EXAMINATION – SUMMER • 2014

		ject Code: X 80905 Date: 31-05-2014 ject Name: Advanced Power Electronics - II	
		ie: 10:30 am - 01:00 pm Total Marks: 70	
	Instr	 uctions: 1. Attempt all questions. 2. Make suitable assumptions wherever necessary. 3. Figures to the right indicate full marks. 	
Q.1	(a)	State different conventional control mechanisms required to control active and reactive power flow of transmission line. Discuss phase-shifting transformer with necessary diagram in brief.	7
	(b)	Write an applications and advantages of FACTS.	7
Q.2	(a) (b)	Explain working of TCR. Draw waveforms of voltage and current for different values of α . Explain the working of TSC-TCR. Draw neat diagrams.	7 7
		OR	_
	(b)	Write a short note on automatic generation control with necessary block diagram.	7
Q.3	(a)	Give comparison of different SVCs	7
Ľ	(b)	Explain load compensation and system compensation with the help of phasor diagram. OR	7
Q.3	(a)	Explain Shunt Compensation for the transmission system.	7
	(b)	Write a short note on TCT.	7
Q.4	(a)	Explain the working of Thyristor Switched Capacitor (TSC). Show with neat diagrams why we cannot use Thyristor Controlled Capacitor (TCC)	7
	(b)	Derive equation showing effect of series compensation on power transfer capability of	7
		transmission line. State advantages and limitations of series compensation.	
		OR	_
Q.4	(a) (b)	Discuss block diagram of pole and converter controllers. Discuss inverter autination angle control (EAC) in brief	7
	(b)	Discuss inverter extinction angle control (EAG) in brief.	7
Q.5	(a)	Explain schematic diagram of HVDC substation and explain working of each component	7
		in brief	
	(b)	State the advantages HVDC transmission over EHVAC transmission for bulk power	7
		transmission.	
OS (a) Discuss following in relation to HVDC link			
Q.5	(a)	 Discuss following in relation to HVDC link. Power flow and current control Power loss in the DC system 	7
	(b)	What is IGBT? Draw its symbol and discuss important features of IGBT. List reason for	7
	<u><u></u></u>	selection of IGBT for VSC based HVDC conversion.	
