Seat No.:	Enrolment No.

GUJARAT TECHNOLOGICAL UNIVERSITY 5

PDDC - SEMESTER- I EXAMINATION – SUMMER 2015			
Subject Name: Elements of Electrical Engineering		Date:02/06/2015 Fotal Marks: 70	
			Instr
	2.	Attempt all questions. Make suitable assumptions wherever necessary. Figures to the right indicate full marks.	
Q.1	(a) (b)		07 e 07
Q.2	(a)	A parallel plate capacitor has a plate area of 4 cm ² . The plates are separated by three slabs of different dielectric materials of thicknesses 0.3, 0.4 & 0.3 mm with relative permittivities of 3, 2.5 and 2 respectively. Calculate the capacitance of each material and the voltage across them in the supply is 200V.	
	(b)	Explain the similarity & dissimilarity between magnetic circuit & electrical circuit.	e 07
	(b)	OR Derive expression for delta to star conversion of resistive network.	e 07
Q.3	(a)	Explain Dynamically induced e.m.f. and Statically induced e.m.f.	1 07
	(b)	Derive the expression for the equivalent capacitance of a group of capacitors when they are connected in (i) series and connected in (ii) parallel. OR	
Q.3	(a)	State and explain laws of electrostatics. Also explain	n 07
	(b)	Electric field intensity. Define the term (i) Reactance (ii) Inductive reactance (iii) Capacitive reactance & discuss how they depend or frequency in a.c. circuit.	07
Q.4	(a)	Explain the phenomena of A.C. through pure inductor with circuit & vector diagram, also prove that active power consumption is zero.	
	(b)	Explain with suitable waveform and vector diagram, the	e 07

generation of three phase EMF.

- Q.4 (a) Explain the resonance phenomena in R-L-C series circuit 07 & derive the equation for resonance frequency.

 Q.4 (b) Define (1) Frequency (2) Time period (3) Phase difference 07
- Q.4 (b) Define (1) Frequency (2) Time period (3) Phase difference 07 (4) Average value (5) Active power (6) Power factor (7) Impedance
- Q.5 (a) A 10 ohm resistor and 20 mH inductor are connected in series across 230 V, 50 Hz supply. Find (i) Circuit impedance (ii) Current (iii) Voltage across resistance & voltage across inductor. (iv) Power factor.
 - (b) Explain the method of measuring three phase power by two watt meters.

OR

- Q.5 (a) Discuss advantages of poly phase system over single phase 07 system.
 - (b) A 415 V, 3-phase voltage is applied to a balanced starconnection connected to 3-phase load of phase impedance (3 +j 4) ohms each. Calculate (i) Line current (ii) Total power supplied.
