Seat No.:	Enrolment No.

## **GUJARAT TECHNOLOGICAL UNIVERSITY**

PDDC - SEMESTER-II EXAMINATION - SUMMER 2015

	Su	<b>Date:</b> 01/06/2015	
	Ti	abject Name: Circuits and Networks  ame: 10.30am-01.00pm  Structions:  1. Attempt all questions. 2. Make suitable assumptions wherever necessary. 3. Figures to the right indicate full marks.	
Q.1	(a) (b)	What is network function? Define the terms "Driving point impedance" and "driving point admittance" of a one port network.  State and explain Millman's theorem.	07 07
Q.2	(a) (b)	Write the property of Laplace Transform (1) Unit impulse (2) Unit step and (3) Unit ramp function Give the application of h-parameter and also state the relation between h-parameter with y-parameter	07 07
	<b>(b)</b>	OR  Derive the symmetry and reciprocity condition for transmission parameter	07
Q.3	(a)	Derive the condition for a maximum power transfer	07
	<b>(b)</b>	Explain any four technique of source transformation	07
Q.3	(a)	<b>OR</b> Explain the concept of Super-node with one suitable example.	07
	<b>(b)</b>	Derive the inter-relationship between incidence matrix, Tie-set matrix and cut-set matrix.	07
Q.4	(a) (b)	Explain the following, (I) co-tree (II) junction (III) loop (IV) Bilateral Element (V) link (VI) Ideal Source Explain the concept of duality.	07 07
		OR	
Q.4	(a)	State and explain reciprocity theorem.	07
	<b>(b)</b>	Derive the initial and final value theorem of Laplace transform.	07
Q.5	(a)	Derive the transient response of series R-L circuit with DC excitation.	07
	<b>(b)</b>	Discuss the rules for drawing a graph and tree	07
Q.5	(a)	OR Write short note on dependent sources.	07
۷.۰			
	<b>(b)</b>	Explain dot convention.	07

\*\*\*\*\*