Seat No.:	Enrolment No.

Subject Code: X31101

GUJARAT TECHNOLOGICAL UNIVERSITY PDDC - SEMESTER-III • EXAMINATION - SUMMER.2015

Date: 29/05/2015

Subject Name: Advance Electronics Time: 02.30pm-05.30pm **Total Marks: 70 Instructions:** 1. Attempt all questions. 2. Make suitable assumptions wherever necessary. 3. Figures to the right indicate full marks. (a) Draw the hybrid -pi model for CE configuration and explain it. **Q.1** 07 (b) Discuss general characteristics of negative feedback amplifier. 07 0.2 (a) Derive the expression for the CE short-circuit current gain A_i as a function of 07 frequency. Define f_{β} and f_{T} . **(b)** Discuss the effect of an emitter bypass capacitor on Low frequency response for 07 single stage CE amplifier. OR (b) When a negative feedback is applied to an amplifier with gain 100, the overall 07 gain reduces to 50. (i) Calculate the fraction of negative feedback (β) (ii) If this fraction is maintained, calculate the value of amplifier gain required if the overall gain with feedback is to be 75. (a) Define Distortion in an amplifier. Explain all type of Distortion. 07 0.3 **(b)** Write a short note on Wien Bridge Oscillator. 07 OR **Q.3** Sketch the high frequency step response of low pass single pole amplifier. 07 (a) Establish the relationship between rise time t_r and high 3 dB frequency f_H. Derive the expression for input and output resistance for Voltage-series feedback 07 **(b)** topology. Write a short note on Barkhausen criteria for sinusoidal oscillation. **Q.4** (a) 07 Define following terms 07 **(b)** (i) Input bias current (ii) Input offset current (iii) Input offset voltage (iv) output offset voltage (v) CMRR (vi) slew rate (vii) PSRR OR (a) What is phase shift oscillator? Draw the circuit diagram of RC phase shift 07 **Q.4** oscillator and derive the equation of frequency of oscillation. What are the characteristics of ideal OP-AMP? Derive the gain of inverting **07 (b)** amplifier. Q.5 (a) Define following terms: 07 (i) Fan in (ii) Fan out (iii) Noise Margin (iv) Propagation delay

	(b)	What is ADC? Mention various types of ADC. Explain successive approximation		
		type ADC.		
		OR		
Q.5	(a)	Why digital to analog conversion is important? Explain weighted register type	07	
		DAC.		
	(b)	Compare DTL, TTL and DCTL logic families.	07	
