Seat No.:	
No	

Enrolment

## **GUJARAT TECHNOLOGICAL UNIVERSITY** PDDC - SEMESTER-V • EXAMINATION – SUMMER 2015

## Subject Code: X50903 Date: 13/05/2015 Subject Name: POWER ELECTRONICS: II Time:02:30 pm - 05:00 pm **Total Marks: 70 Instructions:** 1. Attempt all questions. 2. Make suitable assumptions wherever necessary. 3. Figures to the right indicate full marks. (a) Draw and explain the series Inverter circuit employing Class-A type commutation. 0.1 07 Draw and discuss the important waveforms. List various PWM methods used in inverters for Harmonic reduction and explain **(b)** 07 Sinusoidal Pulse Modulation with necessary waveforms. 0.2 Give the comparison between On/Off control and phase control of A.C voltage 07 (a) controller. **(b)** Explain how the output voltage and frequency of inverter can be controlled? 07 OR Explain selective harmonics elimination method of PWM. How third harmonics can be 07 **(b)** eliminated? 0.3 (a) What is the space vector modulation technique? Compare it with other PWM techniques. 07 Explain single phase voltage controller with R-L load with necessary wave form. 07 **(b)** OR Q.3 Discuss the operation of single phase A.C voltage regulator with R-L load, when $\alpha$ is 07 **(a)** less than or equal to load phase angle $\emptyset$ . Hence show that for $\alpha$ less than the output voltage of A.C voltage regulator cannot be regulated. Explain single phase cyclo-converter with necessary wave form. Give its comparison with 07 **(b)** three phase cyclo-converter. State the various points of comparisons and their choice/criterion for selection between AC **Q.4** 07 **(a)** and DC drives Draw the circuit diagram and explain the working of slip power recovery system using 07 **(b)** solid state scherbius system OR **(a)** Differentiate voltage source inverter with current source inverter. **Q.4** 07 Explain the stator voltage control of induction motor drives. **(b)** 07 **Q.5** Name the different methods of speed control of 3-Ø Induction motor. Explain the **(a)** 07 principle of speed control of it by PWM method. Explain three phase voltage controller with star connected resistive load. **(b)** 07 OR Draw the torque speed characteristics of 3 phase Induction motor and explain the **Q.5** 07 (a) following regions. (1).Plugging (2).Motoring

(b) Give the comparison between On/Off control and phase control of A.C voltage 07 controller

## \*\*\*\*\*