Lnro	lmont
Enro	шеш

Seat No.:	
No	

power supply?

GUJARAT TECHNOLOGICAL UNIVERSITY

PDDC - SEMESTER - VII • EXAMINATION - SUMMER 2015

Subject Code: X70905 Date: 18/05/2015 Subject Name: Advanced Power Electronics – I Time: 02:30 AM to 05:00 PM **Total Marks: 70 Instructions:** 1. Attempt all questions. 2. Make suitable assumptions wherever necessary. 3. Figures to the right indicate full marks. (a) Fill in the blanks. 07 **Q.1** 1) The voltage stress on the controlled switches (IGBTs) of a 3 level NPC inverter is times to that of a conventional two level inverter that operates with the same dc link voltage V_{dc} . 2) A total of _____ switching states are possible to generate five different voltage levels at one leg of a five level cascaded H bridge inverter. clamping capacitors of equal voltage rating are required in one leg of five level flying capacitor inverter. 4) For a general n level NPC inverter, the total number of switching states ____. 5) In general, for an n level (n>=3) NPC inverter, each capacitor has voltage across it equal to_ 6) In a five level cascaded H bridge inverter, the number of DC voltage sources required per leg of the inverter is 7) One leg of n level inverter requires ___ controlled switches of equal voltage rating and neutral point clamping diodes of unequal voltage rating. (b) Explain the two quadrant ZVS converter with relevant diagram and waveform. **07 07** 0.2 (a) How 7 level can be obtained in asymmetric cascaded multi-level inverter? 07 **(b)** Explain parallel resonant inverter circuit with wave form. OR **(b)** With neat circuit diagram and waveform discuss class E resonant inverter. 07 Explain working of five level diode clamped inverter with necessity circuit Q.3 07 (a) diagram and wave forms. **(b)** Compare multi-pulse converter with multi-level inverter. 07 OR Explain working of five level flying capacitor inverter with necessity circuit **Q.3 07** diagram and wave forms. **(b)** Discuss components of UPS. 07 (a) Explain 12 pulse uncontrolled multi-pulse inverter with waveform and diagram. **07 Q.4** What do mean by switch mode power supply? How is it differs from conventional **07 (b)**

Q.4	(a)	Explain working of fly-back type switch mode power supply.	07
	(b)	Discuss push pull converter and its application in dc power supply.	07
Q.5	(a)	Explain difference between sinusoidal and trapezoidal BLDC machine.	07
	(b)	Discuss working principle of SRM. Explain block diagram of SRM drive.	07
		OR	
Q.5	(a)	Discuss control of brushless dc drive. Give its applications.	07
	(b)	Discriminate ON line and OFF line UPS.	07