Seat No.:	Enrolment No.

GUJARAT TECHNOLOGICAL UNIVERSITY PDDC - SEMESTER-VII • EXAMINATION - SUMMER • 2015

Subject Code: X71102 Subject Name: Power Electronics Time:02:30 pm - 05:00 pm Instructions:			Date: 12/05/2015 Total Marks: 70	
		2:30 pm - 05:00 pm Total Marks:		
	2.	Attempt all questions. Make suitable assumptions wherever necessary. Figures to the right indicate full marks.		
Q.1	(a)	Define following terms: (i)Holding current (ii) Turn off time (iii) Reverse recovery charge(iv)Minimum gate current	08	
	(b)	Explain the operation of the SCR using the two transistor analogy. Obtain the condition for the breakdown of the device.	06	
Q.2	(a)	Draw the structure and explain the working principle of the following power devices: (i) Power MOSFET (ii) ICPT	08	
	(b)	(i)Power MOSFET (ii) IGBT What is the purpose of dv/dt protection? Explain the common method of dv/dt protection.	06	
		OR		
	(b)	The thyristors are used in a string to withstand a dc voltage of V_s = 15 kV. The maximum leakage current and recovery charge differences of thyristors are 10mA and 150µC, respectively. Each thyristor has a voltage-sharing resistance of $R = 56k\Omega$ and capacitance of $C_1 = 0.5\mu F$. Determine (a) the maximum steady state voltage sharing $V_{DS(max)}$, (b) the steady-state voltage derating factor, (c) the maximum transient voltage sharing $V_{DT(max)}$, and (d) the transient voltage derating factor.	06	
Q.3	(a) (b)	Explain three-phase half-wave controlled rectifier with resistive load. Describe any two forced commutation methods. OR	07 07	
Q.3	(a)	Describe the operation of single phase dual converters with necessary waveforms.	07	
	(b)	A single phase full converter with RL load uses a delay angle control and is supplied by a 230V-50 Hz input. If $\alpha = \pi/3$, E= 10 V, R= 10 Ω and L = 20 mH, determine the average output voltage, output current, and load impedance.	07	
Q.4	(a)	Explain the principle of operation of step-up chopper. Sketch the current and voltage waveform. Also discuss the modes of operation with equivalent circuit.	07	
	(b)	Explain the working principle of Boost regulator with the help of circuit diagram and waveforms. Draw equivalent circuit for different modes of operation. OR	07	
Q.4	(a)	Show chopper classification. Explain Class C and Class D chopper with necessary diagram.	07	
	(b)	Describe switched mode power supply with necessary diagrams in detail.	07	
Q.5	(a)	What is PWM inverter? Explain its principle and any one method of PWM inverter to control output voltage.	07	
	(b)	Explain battery charger with necessary diagrams. OR	07	

1

- Q.5 (a) Describe the working of single phase bridge inverter with diagram and waveforms.
 - (b) List types of Heating mechanism available and explain any one in detail. 07
