Seat No.:	Enrolment No

## **GUJARAT TECHNOLOGICAL UNIVERSITY**

## **PDDC SEM-II Examination May 2012**

Subject code: X20901 Subject Name: Circuit & Networks

Date: 23/05/2012 Time: 10.30 am – 01.00 pm

**Total Marks: 70** 

<b>T</b> 4	4 •	
Instru	ICT 10	nc
mon a	LUU	115.

1.	Attempt all	questions.
1.	Attempt an	questions

- 2. Make suitable assumptions wherever necessary.
- 3. Figures to the right indicate full marks.

Q.1	(a)	Define the following terms, (I) Link (II) Graph (III) Tree (IV) Node (V) Branch (VI) Super	07
		mesh (VII) Super node	
	<b>(b)</b>	State and explain Maximum Power Transform Theorem when	07
	(~)	load is complex with variable resistance and fixed reactance.	0.
Q.2	(a)	Derive the expression for Y-Parameters for the Parallel	07
	<b>(L)</b>	connection of 2-Two port Networks.	07
	<b>(b)</b>	Find the Z parameter of figure 1.	07
	<b>(b)</b>	OR Find the V peremeter of feature 2	07
	<b>(b)</b>	Find the Y parameter of figure 2.	07
Q.3	(a)	Explain the rules for source transformation technique.	07
Ų.S	(b)	Find the current through 12 $\Omega$ resistor in the network of figure 3	07
	(0)	using node analysis.	07
		OR	
Q.3	(a)	State and Explain Thevenin's Theorem with suitable example.	07
Ų.S	(b)	Find the voltage V suing Superposition theorem of figure 4.	07
	(0)	This the voltage v sunig superposition theorem of figure 4.	07
Q.4	(a)	Explain the concept of the complex frequency.	07
<b>~··</b>	(b)		
	(0)	OR	07
Q.4	(a)	Draw the symbols of : Variac, Inductor, CCVS, VCCS, CCS,	07
	()	VCVS, variable capacitor.	
	<b>(b)</b>	Explain in brief the concept of initial conditions.	07
	()	r	
Q.5	(a)	Prove AB-BC=1.	07
•	<b>(b)</b>	Determine the current through 4 $\Omega$ resistor branch of network	07
	` /	given in figure 6 using mesh analysis.	
		OR	
Q.5	(a)	Classify various sources: CCVS, VCCS, CCCS, VCVS and	07
		explain in detail.	
	<b>(b)</b>	Explain the cascade connection of two nort networks	07

\*\*\*\*\*\*

