Enrolment No._____

GUJARAT TECHNOLOGICAL UNIVERSITY PDDC SEM-II Examination May 2012 Subject code: X20902

Subject Court. 1120, 02 Subject Name: Electrical Measurement I & II Time: 10.30 am – 01.00 pm

Date: 24/05/2012

Instructions:

1. Attempt all questions.

Total Marks: 70

		Make suitable assumptions wherever necessary. Figures to the right indicate full marks.	
Q.1	(a)	Describe the working of Hay's bridge for measurement of Inductance. Derive equation for balance and draw the phasor diagram of bridge under balance conditions.	07
	(b)	Explain Absolute measurement of current by Raileigh's current balance method.	07
Q.2	(a)	Derive the dimensions of the following quantities in L,M,T,I units:1. Potential Gradient2. Capacitance3. Magnetic Flux Density	07
	(b)	Explain two applications of D.C. Potentiometer with necessary circuits. OR	07
	(b)	With neat sketch explain Maxwell inductance capacitance bridge.	07
Q.3	(a) (b)	Explain working principle of induction type energy meter. With phase diagram explain the working principle of current transformer. State its applications.	07 07
		OR	
Q.3	(a)	Which bridge is used for frequency measurement. Draw the circuit for the same.	07
	(b)	Explain construction and working of a basic electronic voltmeter.	07
Q.4	(a)	State the different methods of measuring medium resistances. Explain any one method in brief.	07
	(b)	Explain how the current range of a PMMC instrument can be extended? Also derive equation for shunt.	07
		OR	
Q.4	(a) (b)	Describe different methods of damping with measuring instruments. Prove that the following equation is dimensionally correct. $e = B l v$.	07 07
Q.5	(a) (b)	Describe the Lorentz method for measurement of absolute resistance. Derive the generalized equations for balance of AC Bridge and prove the necessary conditions for bridge balance. OR	07 07
Q.5	(a)	Explain Tri vector meter with a neat diagram.	07
~ "	(b)	Explain Ballistic Galvanometer with diagram.	07 07
