Seat No.:	Enrolment No.

GUJARAT TECHNOLOGICAL UNIVERSITY PDDC-SEMESTER I- • EXAMINATION -WINTER- 2016

U			7/01/2017	
Subject Name: Elements of Electrical Engineering Time: 10:30 AM to 1:00 PM Instructions:		10:30 AM to 1:00 PM Total Marks: 70	Total Marks: 70	
		Attempt all questions. Make suitable assumptions wherever necessary. Figures to the right indicate full marks.		
Q.1	(a) (b)	State and explain Kirchhof's voltage and current laws with suitable examples. Compare electric circuit with magnetic circuit.	07 07	
Q.2	(a) (b)	Explain the method of transforming a delta connected network in star network. Explain the phenomena of rise in current through inductance and derive the equation.	07 07	
		OR		
	(b)	Explain Faraday's laws of electromagnetic induction.	07	
Q.3	(a) (b)	Explain B-H curve for magnetic circuit. Explain the different types of capacitors.	07 07	
	(0)	OR	U1	
Q.3	(a) (b)	Explain resonance in R-L-C series circuit. A certain waveform has a form factor of 1.2 and a peak factor of 1.5. If the maximum value is 100, find rms value and average value.	07 07	
Q.4	(a)	Write the name of methods to solve ac parallel circuits. Explain any one in detail.	07	
	(b)	Define and explain: (i) RMS value (ii) Average value (iii) Peak factor (iv) Form factor (v) Frequency.	07	
0.4	()	OR A Total Control of the Control of	0=	
Q.4	(a)	What are the methods to measure 3-phase power? Explain two wattmeter method in detail.	07	
	(b)	Discuss about the Comparison between series and parallel resonance.	07	
Q.5	(a)	Derive the equation of charging of capacitor. Draw the graph of capacitor voltage and current w.r.t. time.	07	
	(b)	Prove that average power consumed by purely inductive circuit is zero. OR	07	
Q.5	(a)	Derive the relation between line current and phase current in delta and star connection of 3-phase system.	07	
	(b)	A series RLC circuit consists of a resistance of 500 Ohm, inductance of 50 mH and capacitance of 20 pF. Find (i) The resonant frequency (ii) The Q-factor (iii) Half power frequency.	07	
