| Seat No.: | Enrolment No. |
|-----------|---------------|
|           |               |

## GUJARAT TECHNOLOGICAL UNIVERSITY PDDC- SEMESTER III- • EXAMINATION -WINTER- 2016

|     | •                    | t Code: X30902 Date:02/01/201   | 7        |
|-----|----------------------|---|----------|
| Tiı | me: 1<br>truction 1. | t Name: Analog & Digital Electronics  0:30 AM to 1:00 PM  Total Marks: 70  ons:  Attempt all questions.  Make suitable assumptions wherever necessary.  Figures to the right indicate full marks. | 0        |
| Q.1 | (a)<br>(b)           | Enlist Characteristics of ideal Op-Amp.  Define Following  (1)Slew Rate (2) Input offset voltage (3) Input bias current.  (4) Open loop voltage gain.(5) CMRR (6) PSRR (7) Input offset current   | 07<br>07 |
| Q.2 | (a)<br>(b)           | Explain Op-Amp as a Comparator.  Explain 555 timers as an Astable Multivibrator with necessary Equations.  OR   | 07<br>07 |
|     | <b>(b)</b>           | Explain 555 timers as an Monostable Multivibrator with necessary Equations.   | 07       |
| Q.3 | (a)<br>(b)           | Enlist Truth Tables of All Logic Gates. Convert following into binary number (1)(85.63) <sub>10</sub> (2) (436) <sub>8</sub>  | 07<br>07 |
|     |                      | OR  |          |
| Q.3 | (a)<br>(b)           | Explain Importance of K-map With Example.  Convert following number into gray code (1)(1011) <sub>2</sub> (2) (46) <sub>10</sub>  | 07<br>07 |
| Q.4 | (a)<br>(b)           | Compare Performance Characteristic of Digital Logic Families.  Minimize the following Boolean expression using K-map and realize it using the basic gates  Y=Em(1,3,5,9,11,13)                    | 07<br>07 |
|     |                      | OR  |          |
| Q.4 | (a)                  | Why NOR and NAND gates are known as universal gate? Make OR and AND   | 07       |
|     | <b>(b)</b>           | gate using NOR and NAND gates.  Minimize the following Boolean expression using K-map and realize it using the basic gates  Y=Em(1,2,9,10,11,14,15)   | 07       |
| Q.5 | (a)<br>(b)           | Describe J-K flip flop. How J-K flip-flop differ from S-R flip-flop? Classify counters and explain One of them.  OR   | 07<br>07 |

\*\*\*\*\*

**Q.5** (a) Compare D-Flip Flop with T-Flip Flop.

**(b)** Classify registers and explain One of them.

**07** 

**07**