GUJARAT TECHNOLOGICAL UNIVERSITY PDDC- SEMESTER III- • EXAMINATION -WINTER- 2016

Subject Code: X31101 Subject Name: Advance Electronics Time:10:30 AM to 1:00 PM Instructions:

Date:30/12/2016

Total Marks: 70

- 1. Attempt all questions.
- 2. Make suitable assumptions wherever necessary.
- 3. Figures to the right indicate full marks.
- **Q.1** (a) Draw and explain Hybrid- π model for CE transistor configuration. 07
 - (b) For CE short circuit current gain g_m = 50 mA/V, $r_{b'e}$ = 1 K Ω , C_e = 1 pF and C_c = 07 0.2 pF, determine the values of f_β and f_T .
- Q.2 (a) Draw RC coupled Amplifier using Common emitter configuration. Obtain 07 equation for lower 3-db frequency for the same circuit.
 - (b) Three cascaded stage have an overall upper 3 dB frequency of 16 KHz and lower 3 dB frequency of 25 Hz. Find the value of F_L and F_H of each stage. Assume that all the stage are identical. Also calculate bandwidth of each stage.

OR

(b) What is Oscillator? Which condition should be full filled for oscillation. 07 Explain that condition also.

Q.3	(a)	Draw and explain working of Hartley oscillator.	07
	(b)	Draw and explain working of Wein bridge oscillator.	07
		OR	
Q.3	(a)	Define Feedback. List and explain types of feedback. List advantages and disadvantages of them.	07
	(b)	Explain Voltage series feedback topology with suitable example.	07
Q.4	(a)	Define op amp. Draw and explain block diagram of op amp. List characteristics for ideal op amp.	07
	(b)	Explain significance of pole zero compensation for op amp with suitable diagram.	07
OR			
Q.4	(a)	 Define following terms with reference to opamp 1) Output offset voltage 2) CMRR 3) Slew rate 4) Input bias current 5) Differential Amplifier 6) PSRR 7) Thermal drift 	07
	(b)	Give comparisons between different logic families.	07
Q.5	(a)	Explain TTL with suitable example.	07
	(b)	Explain R-2R ladder type DAC.	07
		OR	
Q.5	(a)	Explain dual slope A/D converter.	07
	(b)	Explain Successive approximation ADC.	07
